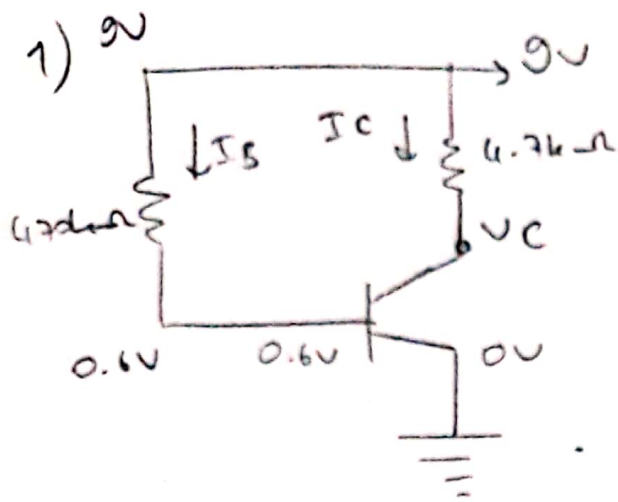


Boşun Aggildir  
1901061252  
B. Appled




$$I_B = \frac{9 - 0.6}{4.7} = 0.017 \text{ mA}$$

$$I_C = \beta \cdot I_B = 0.893 \text{ mA}$$

$$V_C = 9 - (0.893) \cdot 4.7 = 4.8 \text{ V}$$


$$V_{CE} = 4.8 - 0 = 4.8 \text{ V}$$

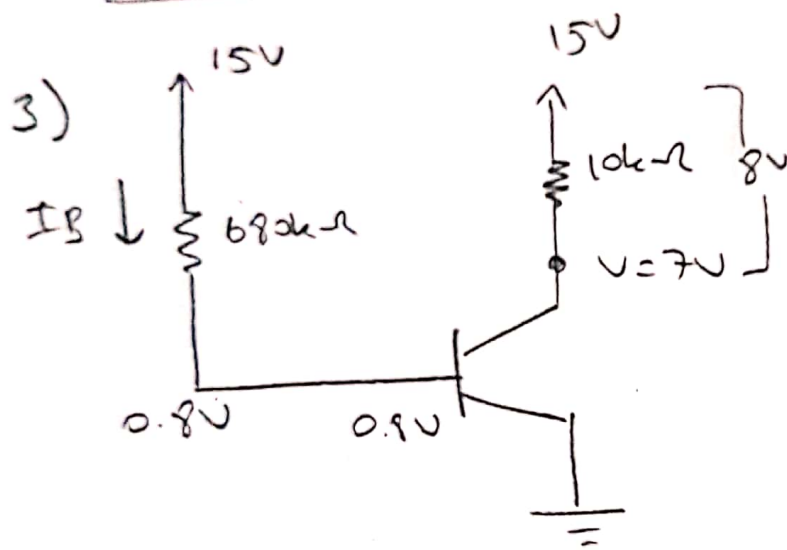

$$I_C = \frac{8}{10} = 0.8 \text{ mA}$$

$$I_B = \frac{15 - 0.8}{680} = 0.021 \text{ mA}$$

$$\beta = \frac{I_C}{I_B} = 38.3$$

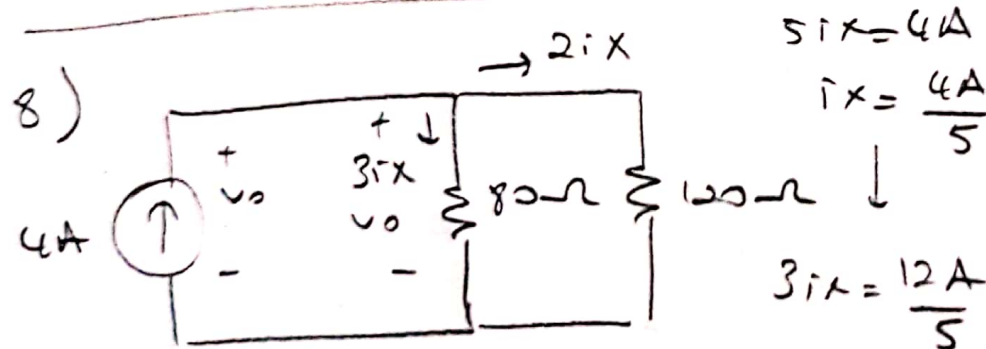


$$5ix = 4 \text{ A}$$

$$ix = \frac{4 \text{ A}}{5}$$

$$3ix = \frac{12 \text{ A}}{5}$$

$$V_0 = \frac{12 \text{ A}}{5} \cdot 80 \Omega$$

$$V_0 = 192 \text{ V}$$

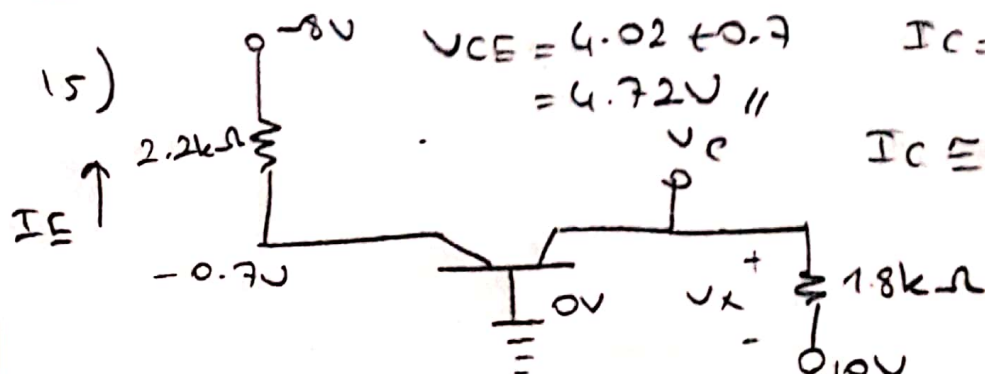

$$V_{CE} = 4.02 + 0.7 = 4.72 \text{ V}$$

$$I_C = \frac{7.3}{2.2} = 3.32 \text{ mA}$$

$$I_C \approx I_E = 3.32 \text{ mA}$$


$$V_X = 3.32 \times 1.8$$

$$V_X = 5.98 \text{ V}$$


$$V_C = 10 - 5.98$$

$$V_C = 4.02 \text{ V}$$

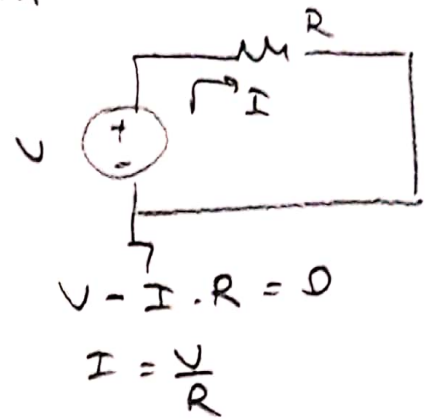
21) By the Kirchhoff's Voltage Law (KVL) sum of the voltages in a circuit is zero  $\sum_{i=1}^n V_i = 0$



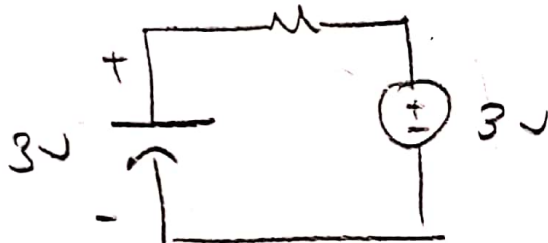
13) After many time, capacitor stores all the voltage  
It acts like an open circuit



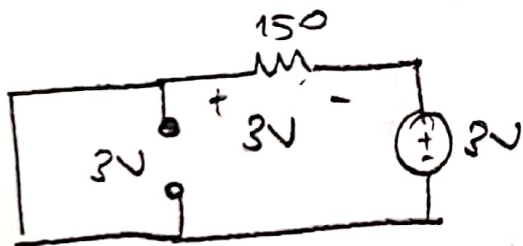14) At steady stage  $t > 0$   $V_{150\Omega} = 3V$



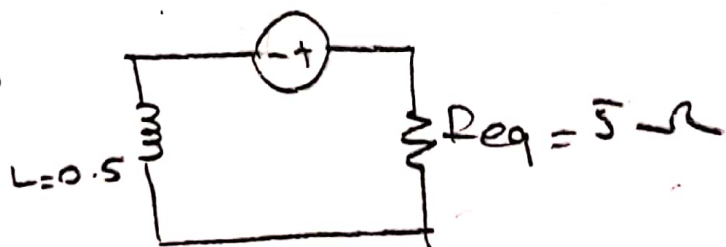
9)  $\uparrow = \frac{L}{R}$  for  $t > 0$



$$\uparrow = \frac{0.5}{5} = 0.1 \text{ s} = 10 \text{ ms}$$

Baris Aygildiz  
1901062252  
B. Aygildiz

10) for  $t < 0$ , steady state

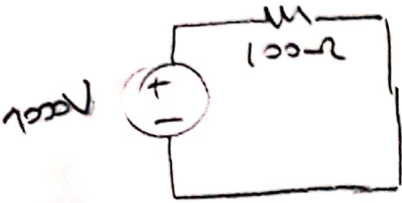


$$I_L = 10 \text{ A} \rightarrow i(0)$$

$$i(0) = 10 \text{ A}$$

$$i(\infty) = -20 \text{ A}$$

$$i(t) = 10 e^{-t/\tau}$$

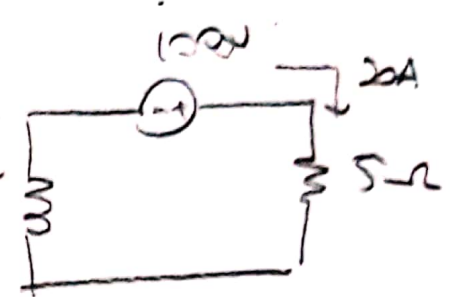

$$i(t) = (-20 + 30 e^{-t/\tau}) \text{ A}$$

$$i(0) = 10 \text{ A}, i(\infty) = -20 \text{ A}$$

19)  $\alpha = \frac{R}{2L}$ ,  $\omega_0 = \sqrt{\frac{1}{LC}}$   $\alpha = \omega_0$  (critically damped)

$$\frac{R}{2 \cdot 125 \times 10^{-3}} = \sqrt{\frac{1}{125 \times 10^{-3} \cdot 0.32 \times 10^{-6}}}$$


$$\frac{R \cdot 10^3}{250} = \sqrt{\frac{10^8}{44}} = \frac{10^4}{2}$$

$$\frac{R \cdot 10^3}{250} = 5000 \Rightarrow 4R = 50000$$

$$R = 1250 \Omega$$

Boris Aygildir 1901062051  
B. Aygildir

20)

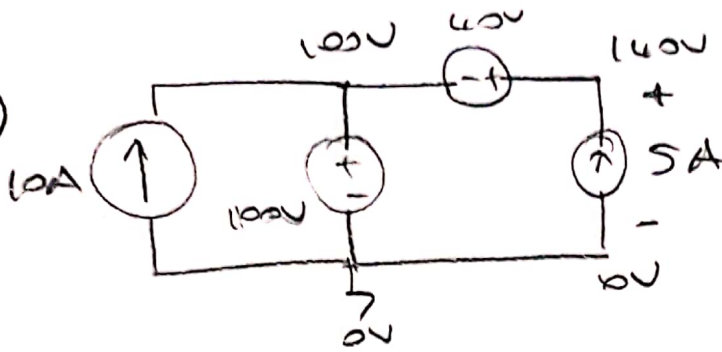


$$P = 1V$$

$$P = -5.140$$

$$P = -700W$$

23)

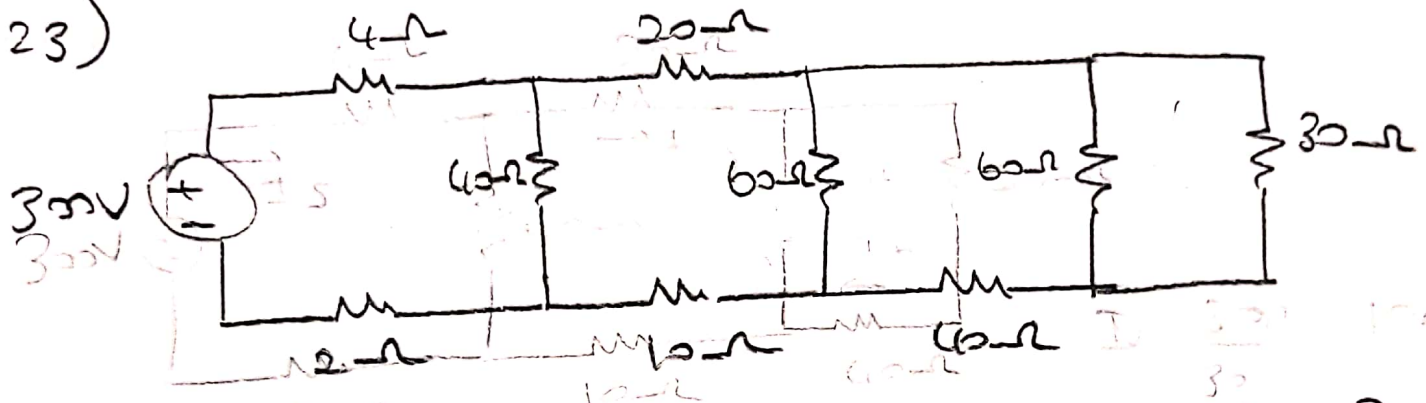

$$R_{eq} = \left[ (60 \parallel 30 + 40) \parallel 60 + 30 \right] \parallel 40 + 6 = 30\Omega$$


$$I = \frac{300}{30} = 10A$$

$$51K = 10A$$

$$2ix = 4A$$

$$2A$$


$$I_6 = 2A$$

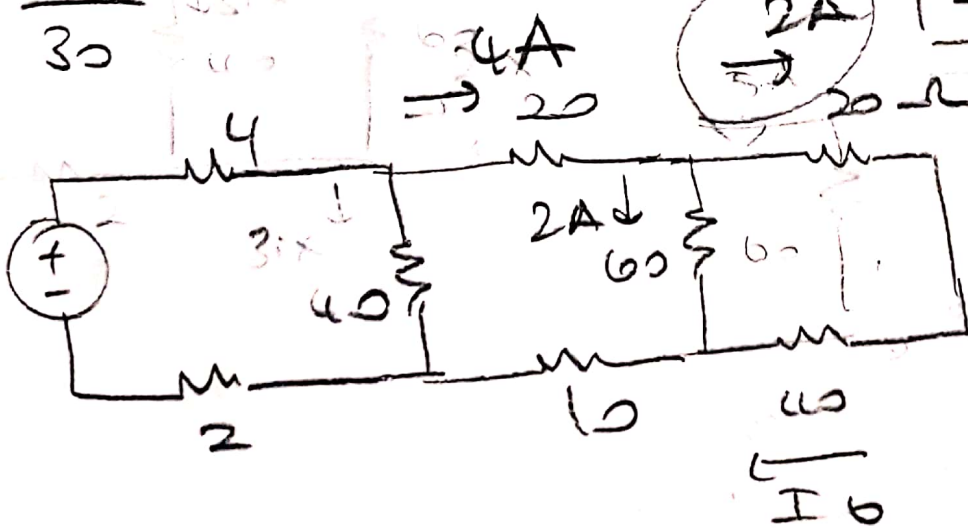

Boris Aygildir

1901042252

B. Aygildir

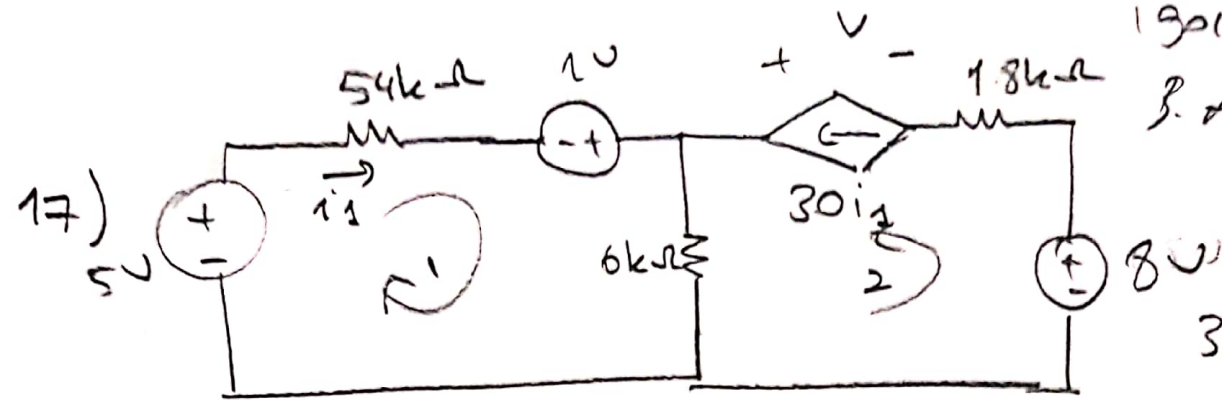

$$30i_1 = 0.75 \text{ A}$$

loop 1

$$5 - 54i_1 + 1 - 31i_1 \cdot 6 = 0$$

$$6 = 240i_1$$

$$i_1 = 0.025 \text{ A}$$


loop 2

$$8 - (1.8)(0.75)$$

$$+ V - (31i_1) \cdot 6 = 0$$

$$\Rightarrow 6.65 + V - 4.65 = 0$$

$$V = -2 \text{ V}$$

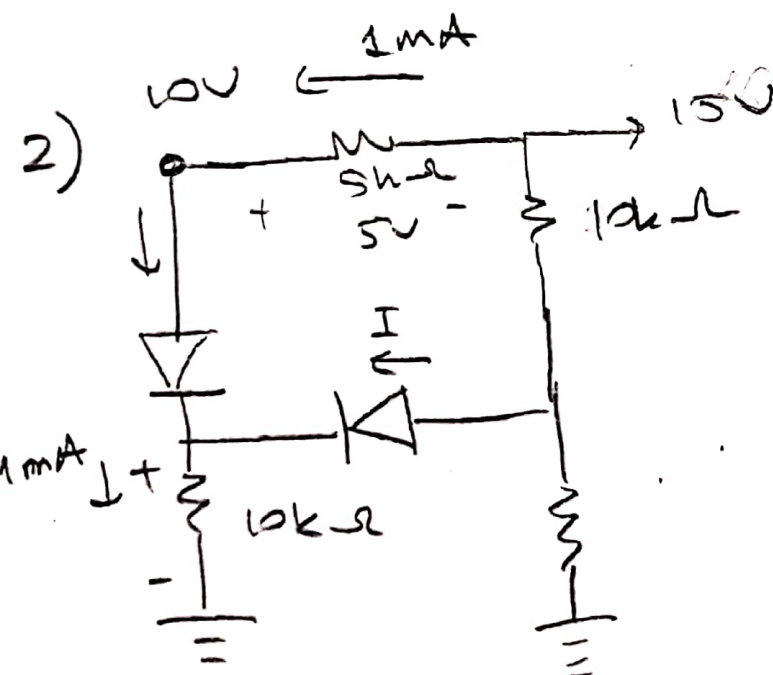

$$I = 0 \text{ A}$$

↓

$$D_2 = \text{OFF}$$

$$D_1 = \text{ON} \text{ (1mA goes through)}$$

$$V = 15 - 5k\Omega \cdot 1\text{mA}$$

$$V = 10 \text{ V}$$

$$19) \frac{V_1 - V_2}{R_1 + R_2} + \frac{V_1}{R_2} + \frac{V_1 - V_2}{R_3} = 0$$