

4-1) a) 12 branches

b) All the branches except the one with 25 mA current source.


c) 10 essential branches

d) 9 essential branches (except the current source)

e) 7 nodes

f) 5 essential nodes

g) 6 meshes

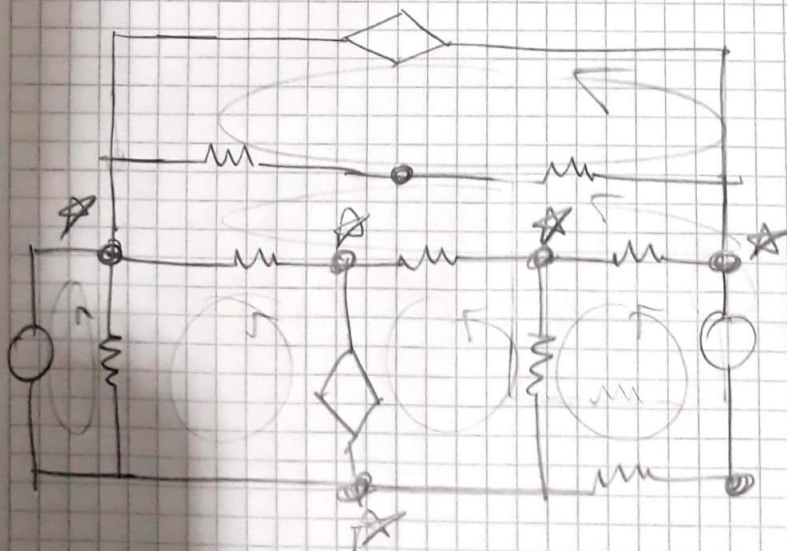

4-2) a) 9 equations for 9 essential branches

b) KCL formula  $\rightarrow (n - 1) = 5 - 1 = 4$  equations  
node

c)  $b - 4 = 9 - 4 = 5$  equations

4-3) a)  $V_S$  and  $R_1$  has the same current,

$R_4$  and  $R_6$  has the same current and


$R_5$  and  $R_7$  has the same current

$\Rightarrow 8$  (different components)  $8 - 3 = 5$  different unknown currents

b) There are 3 essential nodes

$n_e - 1 = 2$  independent KCL equations


c)

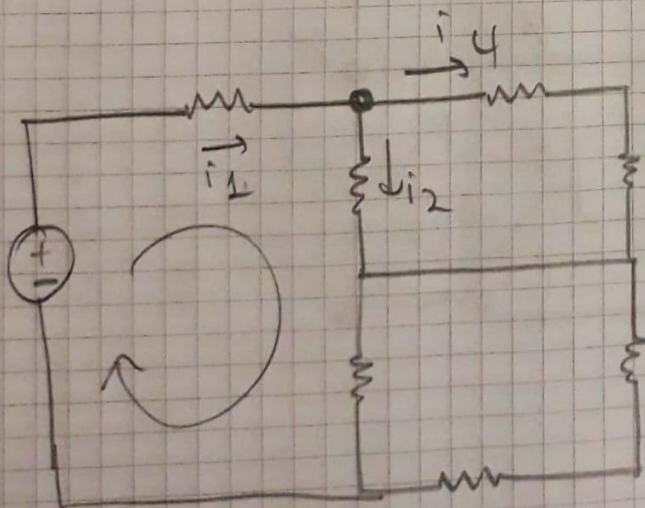


d) 3 for 3 meshes

e)  $V_S - R_1 i_2 - R_2 i_2 - R_3 i_3 = 0$

$$-i_1 + i_2 + i_4 = 0$$

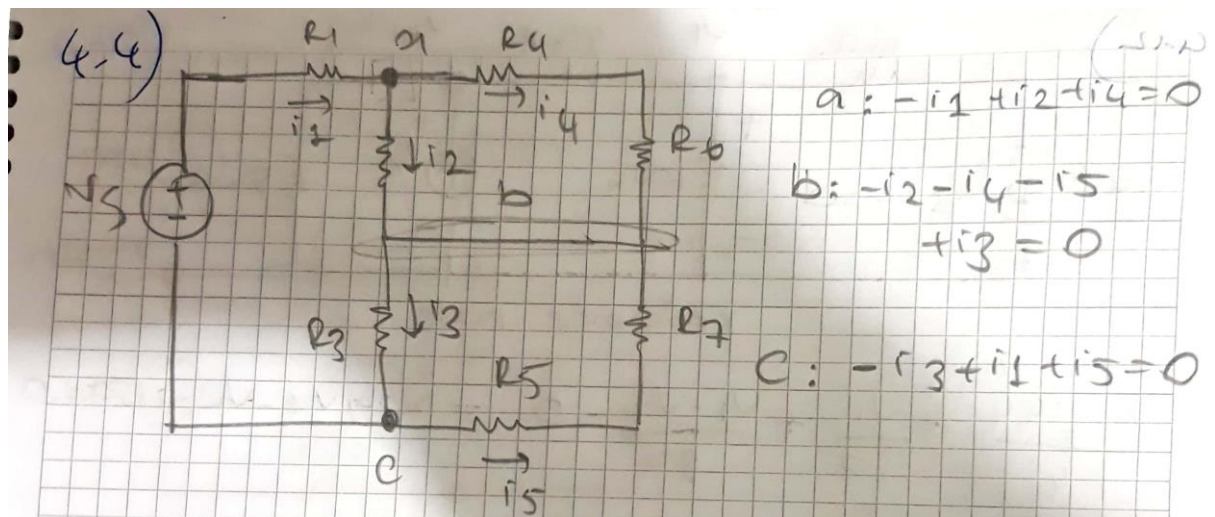



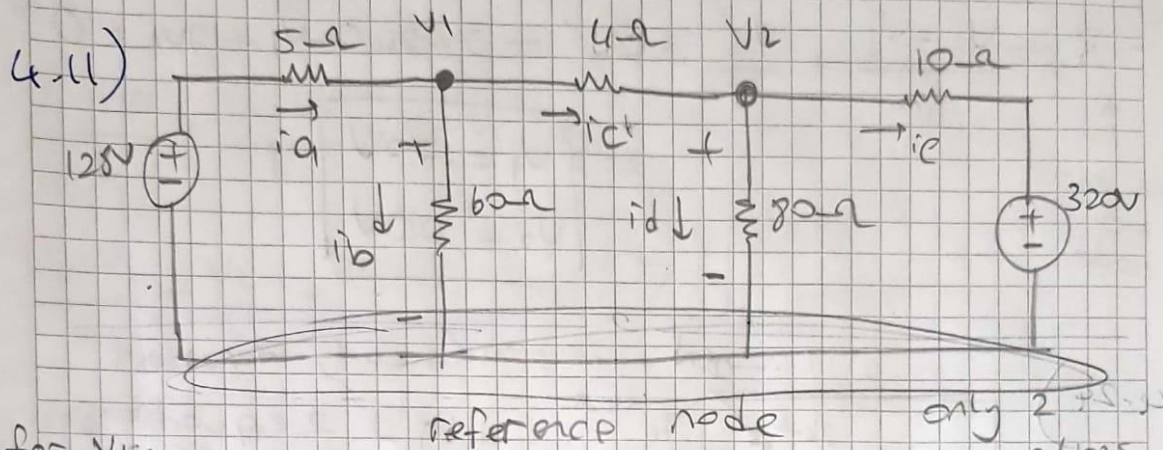

for  $V_1$ :

$$\frac{V_1 - 128}{5} + \frac{V_1}{60} + \frac{V_1 - V_2}{4} = 0 \Rightarrow 12V_1 - 1536 + V_1 + 15V_1 - 15V_2 = 0$$

$$28V_1 - 15V_2 = 1536$$

for  $V_2$ :

$$\frac{V_2 - V_1}{4} + \frac{V_2}{80} + \frac{V_2 - 320}{10} = 0 \Rightarrow 20V_2 - 20V_1 + V_2 + 8V_2 - 2560 = 0$$

$$-20V_1 + 29V_2 = 2560$$

$$i_a = \frac{128 - 162}{5} = -6.8A$$

$$i_b = \frac{162}{60} = 2.7A$$

$$i_c = \frac{162 - 200}{4} = -9.5A$$

$$i_d = \frac{200}{80} = 2.5A$$

$$i_e = \frac{200 - 320}{10} = -12A$$

$$\Rightarrow \begin{array}{l} 28V_1 - 15V_2 = 1536 \quad | \cdot 29 \\ -20V_1 + 29V_2 = 2560 \quad | \cdot 28 \end{array}$$


$$-300V_2 + 812V_2 = 102400$$

$$V_2 = 200V$$

$$V_1 = 162V$$

$$P_{320V} = i_e \cdot 320 = (-12) \cdot 320$$
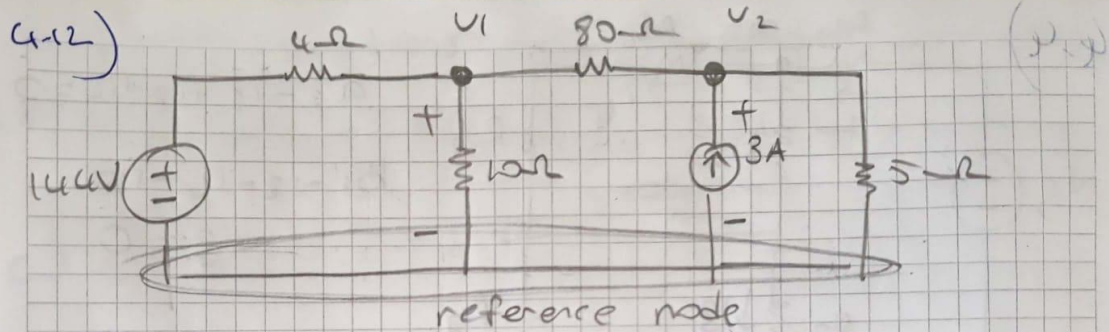
$$= -3840W \quad (3840W \text{ developed})$$



$$\frac{V_1 - 144}{4} + \frac{V_1}{10} + \frac{V_1 - V_2}{80} = 0 \Rightarrow 20V_1 - 2880 + 9V_1 + V_1 - V_2 = 0$$

$$29V_1 - V_2 = 2880$$

$$\frac{V_2 - V_1}{80} + \frac{V_2}{5} - 3 = 0 \Rightarrow V_2 - V_1 + 16V_2 - 240 = 0$$

$$-V_1 + 17V_2 = 240 \quad (2)$$


$$29V_1 - V_2 = 2880$$

$$-29V_1 + 493V_2 = 6960$$

$$\begin{array}{|l} V_1 = 100V \\ V_2 = 20V \end{array}$$

$$\leftarrow 492V_2 = 9840$$



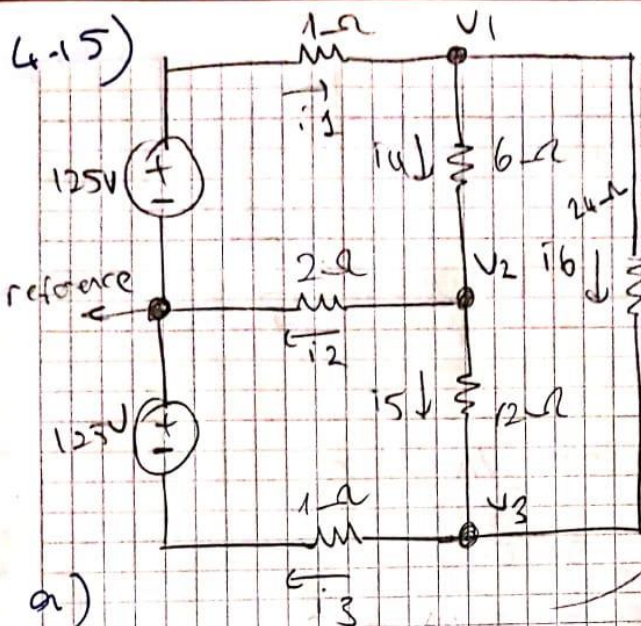

$$29V_1 - 11V_2 - V_3 = 3000$$

$$-2V_1 + 9V_2 - V_3 = 0$$

$$-V_1 - 2V_2 + 27V_3 = -3000$$

$$\begin{bmatrix} 29 & -4 & -1 \\ -2 & 9 & -1 \\ -1 & -2 & 27 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 3000 \\ 0 \\ -3000 \end{bmatrix}$$

$$Ax = b$$

$$x = A^{-1}b$$

$$x = \begin{bmatrix} 101.24 \\ 10.66 \\ -106.57 \end{bmatrix} \begin{matrix} V_1 \\ V_2 \\ V_3 \end{matrix}$$

a)

$$\frac{V_1 - 125}{1} + \frac{V_1 - V_2}{6} + \frac{V_1 - V_3}{24} = 0$$

$$\frac{V_2 - V_1}{6} + \frac{V_2}{2} + \frac{V_2 - V_3}{12} = 0$$

$$\frac{V_3 + 125}{1} + \frac{V_3 - V_2}{12} + \frac{V_3 - V_1}{24} = 0$$

$$i_1 = \frac{125 - 101.24}{1} = 23.76 \text{ A}$$

$$i_2 = \frac{10.66}{2} = 5.33 \text{ A}$$

$$i_3 = \frac{-106.57 + 125}{1} = 18.43 \text{ A}$$

$$i_4 = \frac{101.24 - (10.66)}{6} = 15.10 \text{ A}$$

$$i_5 = \frac{10.66 - (-106.57)}{12} = 9.77 \text{ A}$$

$$i_6 = \frac{101.24 - (-106.57)}{24} = 8.66 \text{ A}$$

b) battery

$$P_{dev} = 125(23.76) + 125(18.43)$$


$$P_{dev} = 5273.75 \text{ W}$$

resistors

$$P_{dis} = (23.76)^2 \cdot 1 + (5.33)^2 \cdot 2 + (18.43)^2 \cdot 1 + (15.10)^2 \cdot 6 + (9.77)^2 \cdot 12 + (8.66)^2 \cdot 24$$

$$= 5273.75 \text{ W}$$

4.27)

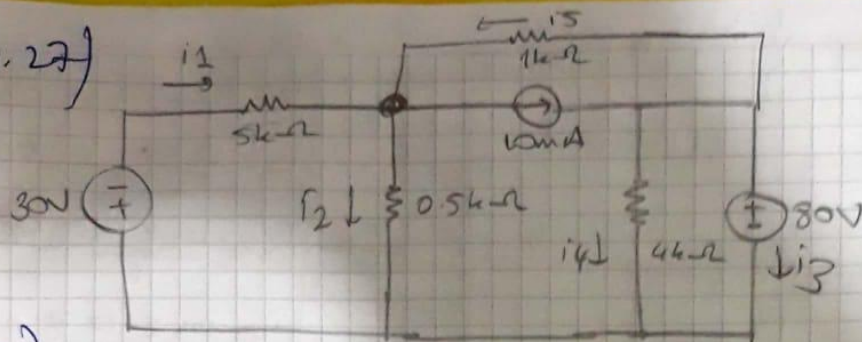

a)

$$\frac{V_A + 30}{5000} + \frac{V_A - 80}{1000} + 0.01 + \frac{V_A}{500} = 0$$

(5)                      (10)

$$\Rightarrow V_A + 30 + 10V_A - 400 + 50 + 5V_A = 0$$

$$\Rightarrow 16V_A = 320$$

$$\boxed{V_A = 20V}$$

$$i_1 = (30 - 20) / 5000 = -10 \text{ mA}$$

$$i_2 = 20 / 500 = 40 \text{ mA}$$

$$i_4 = 80 / 4000 = 20 \text{ mA}$$

$$i_5 = (80 - 20) / 1000 = 60 \text{ mA}$$

$$i_3 = 10 \text{ mA} - i_4 - i_5 \Rightarrow i_3 = -70 \text{ mA}$$

$$b) P_{30V} = 30(-0.01) = -0.3 \text{ W}$$

$$P_{80V} = 80(-0.07) = -5.6 \text{ W}$$

$$P_{10mA} = (-60)(0.01) = -0.6 \text{ W}$$

$$+ \underline{\quad\quad\quad}$$

$$6.5 \text{ W}$$

$$P_{4k} = 80^2 / 4000 = 1.6 \text{ W}$$

$$P_{1k} = 60^2 / 1000 = 3.6 \text{ W}$$

$$P_{500} = (0.04)^2 \cdot 500 = 0.8 \text{ W}$$


$$P_{5k} = (0.01)^2 \cdot 5000 = 0.5 \text{ W}$$

$$+ \underline{\quad\quad\quad}$$

$$6.5 \text{ W}$$



4.30)

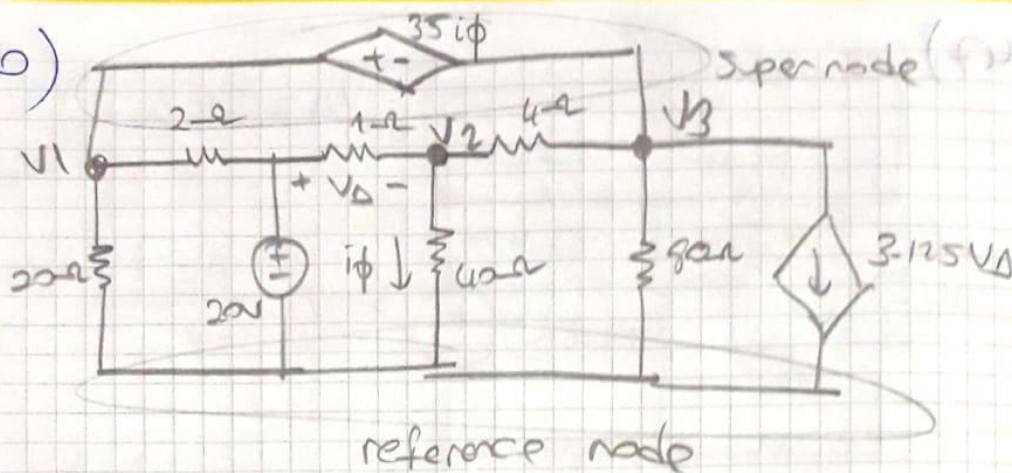

from supernode:

$$\frac{V_3 - V_2}{4} + \frac{V_3}{80} + 3.125 + \frac{V_1}{20} + \frac{V_1 - 20}{2} = 0$$

from  $V_2$ :

$$\frac{V_2 - V_3}{4} + \frac{V_2 - 20}{1} + \frac{V_2}{40} = 0$$

$$\cancel{80} \frac{V_3}{4} - \frac{V_2}{4} + \frac{V_3}{80} + 3.125 + \frac{V_1}{20} + \frac{V_1}{2} - 10 = 0$$

$$\cancel{40} \frac{V_2}{4} - \frac{V_3}{4} + V_2 - 20 + \frac{V_2}{40} = 0$$

=> after solving the equations ---

$$V_1 = -20.25V, V_2 = 10V, V_3 = -29V$$


current over 20V source

$$i_{20V} = \frac{-20.25}{2} + \frac{10}{1} = 30.125A$$

$$P = 20(30.125) = 602.5W$$



4-36)

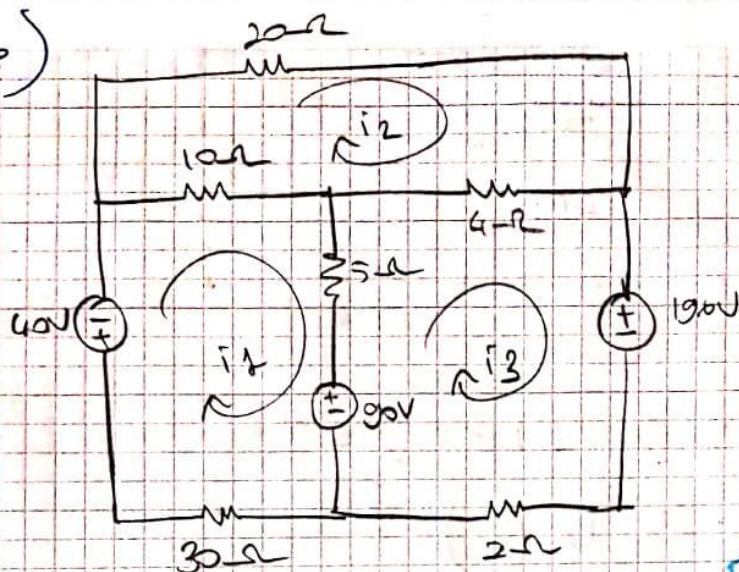

$$-40 + 10(i_1 - i_2) + 5(i_1 - i_3) + 90 + 30i_1 = 0$$

$$20i_2 + 4(i_2 - i_3) + 10(i_2 - i_1) = 0$$

$$190 + 2i_3 - 90 + 5(i_3 - i_1) + 4(i_3 - i_2) = 0$$

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -5 \\ -3 \\ -13 \end{bmatrix}$$

$$45i_1 - 10i_2 - 5i_3 = -130$$

$$-10i_1 + 34i_2 - 4i_3 = 0$$

$$-5i_1 - 4i_2 + 11i_3 = -106$$

$$\Rightarrow \begin{bmatrix} 45 & -10 & -5 \\ -10 & 34 & -4 \\ -5 & -4 & 11 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -130 \\ 0 \\ -106 \end{bmatrix}$$

$$a) P_{40V} = 40(-5) = -200W \text{ (delivered)}$$

$$P_{90V} = 90(-5 - (-13)) = 720W \text{ (absorbed)}$$

$$P_{190V} = 190(-13) = -2470W \text{ (delivered)}$$

$$P_{Del} = 2748W$$

$$b) P_{4\Omega} = 400W$$

$$P_{5\Omega} = 320W$$

$$P_{30\Omega} = 750W$$

$$P_{10\Omega} = 40W$$

$$P_{20\Omega} = 180W$$


$$P = IV = I^2 R$$

$$P_{2\Omega} = 338W$$

+


$$2748W$$

4-39)

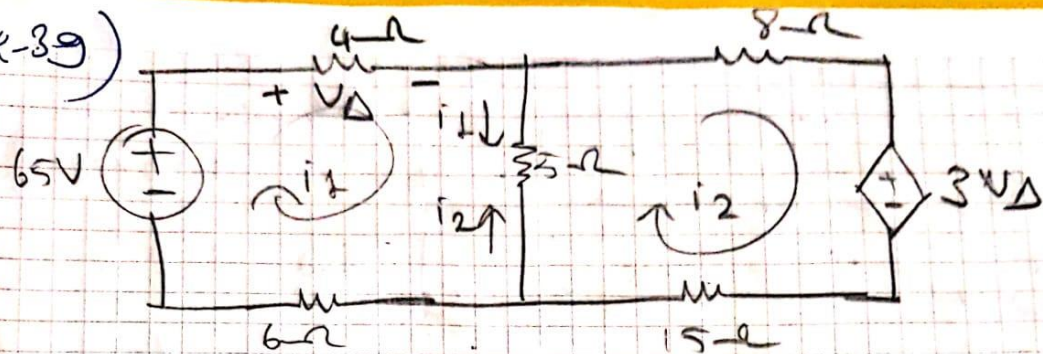

$$65 - 4i_1 - 5(i_2 - i_1) - 6i_1 = 0$$
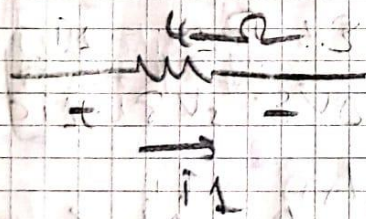
$$-3V_{\Delta} - 15i_2 - 5(i_1 - i_2) - 8i_2 = 0$$



$$V_{\Delta} = 4i_1$$


$$\begin{cases} i_1 = 4A \\ i_2 = -1A \\ V_{\Delta} = 16V \end{cases}$$

$$P = i^2 R$$

$$P_{15\Omega} = (-1)^2 \cdot 15 = 15W$$



4.4b)

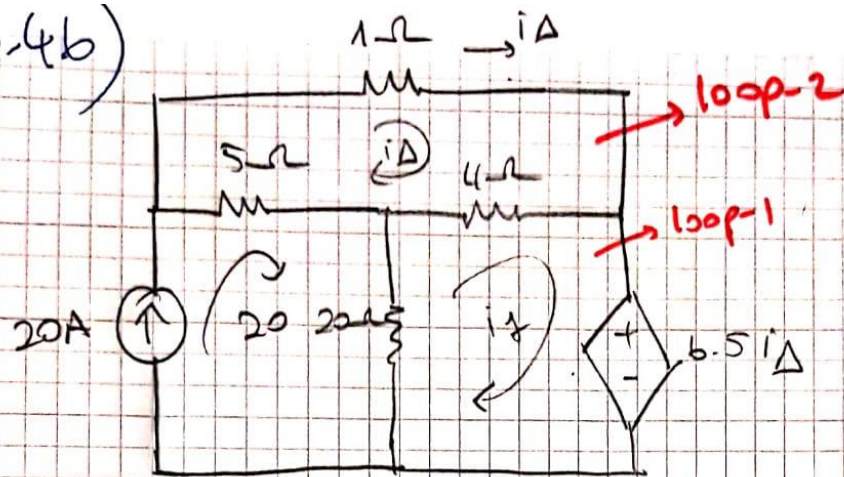

$$\textcircled{1} \quad 20i_1 - 400 + 4i_1 - 4i_\Delta + 6.5i_\Delta = 0$$

$$24i_1 + 2.5i_\Delta = 400$$

$$\textcircled{2} \quad 10i_\Delta - 4i_2 = 100 \quad | \times 6$$


$$\Rightarrow 62.5i_\Delta = 1000 \Rightarrow \boxed{i_\Delta = 16 \text{ A}} \quad | \quad \boxed{i_2 = 15 \text{ A}}$$

Total power developed by 20A current source :

$$V_{20A} = 1i_\Delta + 6.5i_\Delta = 120 \text{ V}$$

$$P_{20A} = 20 \cdot 120 = 2400 \text{ W}$$

1.47)

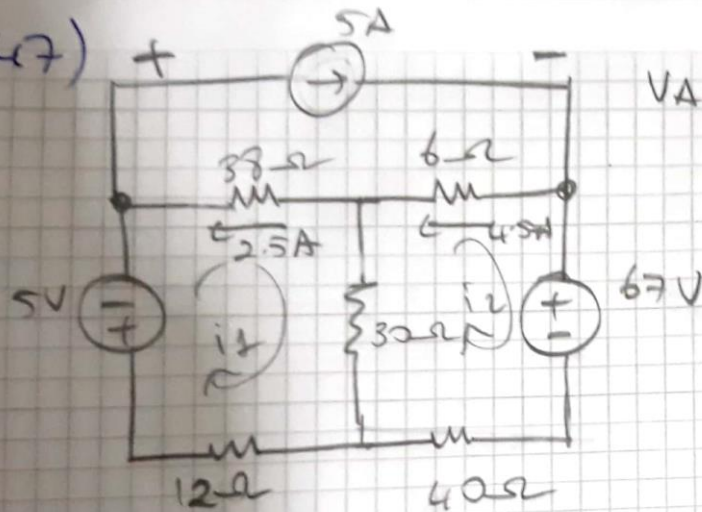

$$V_A = 38(2.5) + 6(4.5)$$

$$V_A = 122V$$

$$+5 + 38(i_1 - 5) + 30(i_1 - i_2) + 12i_1 = 0$$


$$67 + 40i_2 + 30(i_2 - i_1) + 6(i_2 - 5) = 0$$

$$\Rightarrow \boxed{i_1 = 2.5A} \quad \boxed{i_2 = 0.5A}$$

$$P_{5A} = V_{5A} \cdot 5 = 122 \cdot 5 = 610W \quad (\text{uses } 610W) \\ \downarrow \\ \text{absorbed}$$



4.54)

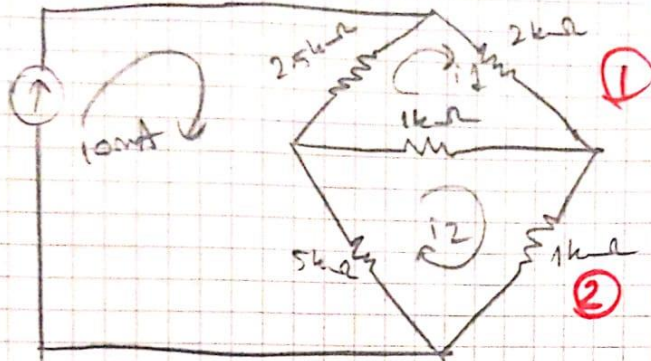

$$\textcircled{1} \quad 2500i_1 - 2500(0.01) + 1000i_1 - 1000i_2 + 2000i_1 = 0$$

$$5500i_1 - 1000i_2 = 25$$

$$\textcircled{2} \quad 3000i_2 - 50 + 1000i_2 - 1000i_1 + 1000i_2 = 0$$

$$7000i_2 - 1000i_1 = 50$$

$$\Rightarrow i_1 = 6\text{mA}, i_2 = 8\text{mA}$$


$$i_{1k} = -2\text{mA}$$

$$P_{1k} = (-0.002)^2 (1000) = 4\text{mW}$$

$$P_{10mA} = (2000i_1 + 1000i_2) \times (0.01)$$

$$P_{10mA} = 200\text{mW}$$

↓ developed

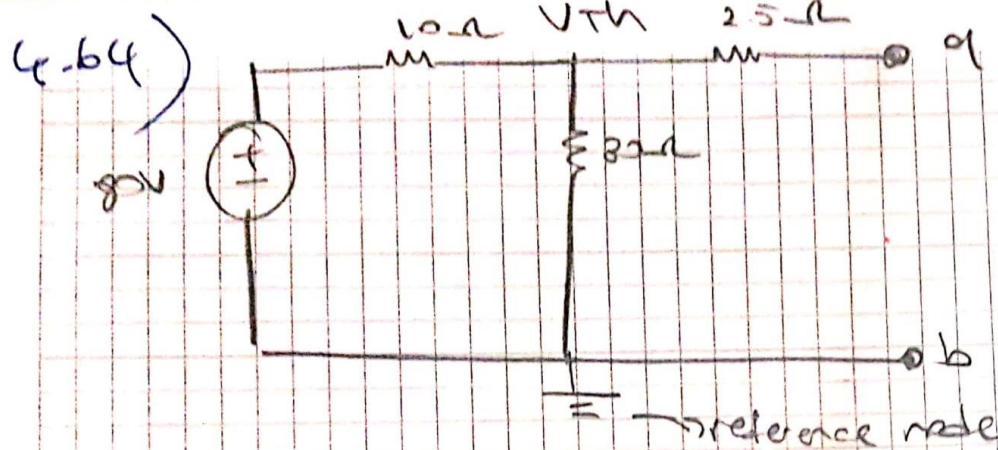

$$\frac{V_{TH} - 80}{10} + \frac{V_{TH}}{30} = 0$$


(3)

$$\Rightarrow 3V_{TH} - 240 + V_{TH} = 0 \Rightarrow V_{TH} = 240$$

$$\boxed{V_{TH} = 60V}$$



4-78)

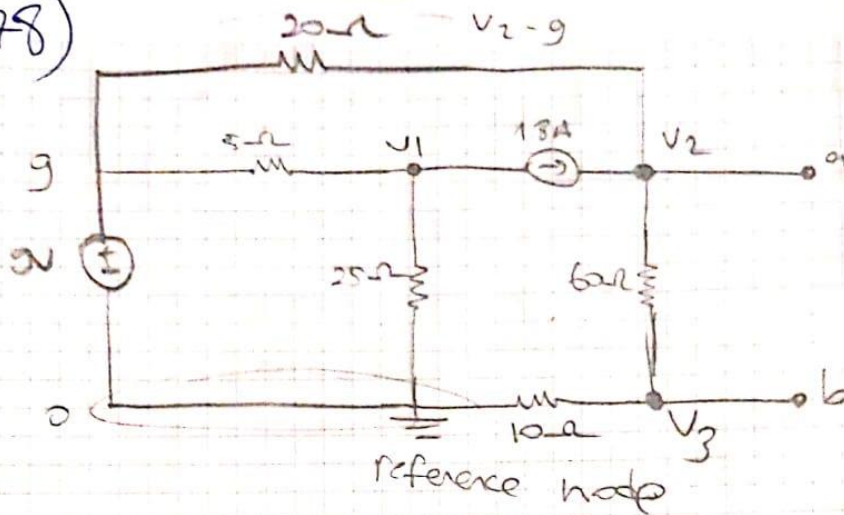

$$\frac{V_2}{70} + \frac{V_2 - 9}{20} - 1.8 = 0$$

$$\Rightarrow |V_2 = 35V|$$

↓


$$V_{ab} = V_{Th} = 30V$$

$$\frac{V_3 - V_2}{60} + \frac{V_3}{10} = 0$$

$$\frac{V_3 - 35}{60} + \frac{6V_3}{10} = 0$$

$$\Rightarrow 7V_3 = 35$$

$$|V_3 = 5V|$$

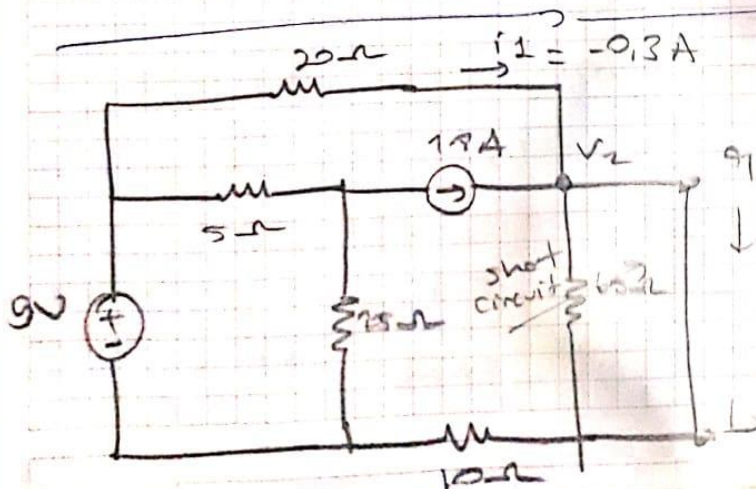

with nodal analysis

$$\Rightarrow |V_2 = 15V|$$


$$|i_2 = 1.5A|$$

$$R_{in} = \frac{30}{1.5}$$


$$R_{Th} = 20\Omega$$

# Simulations


## 4.11.a

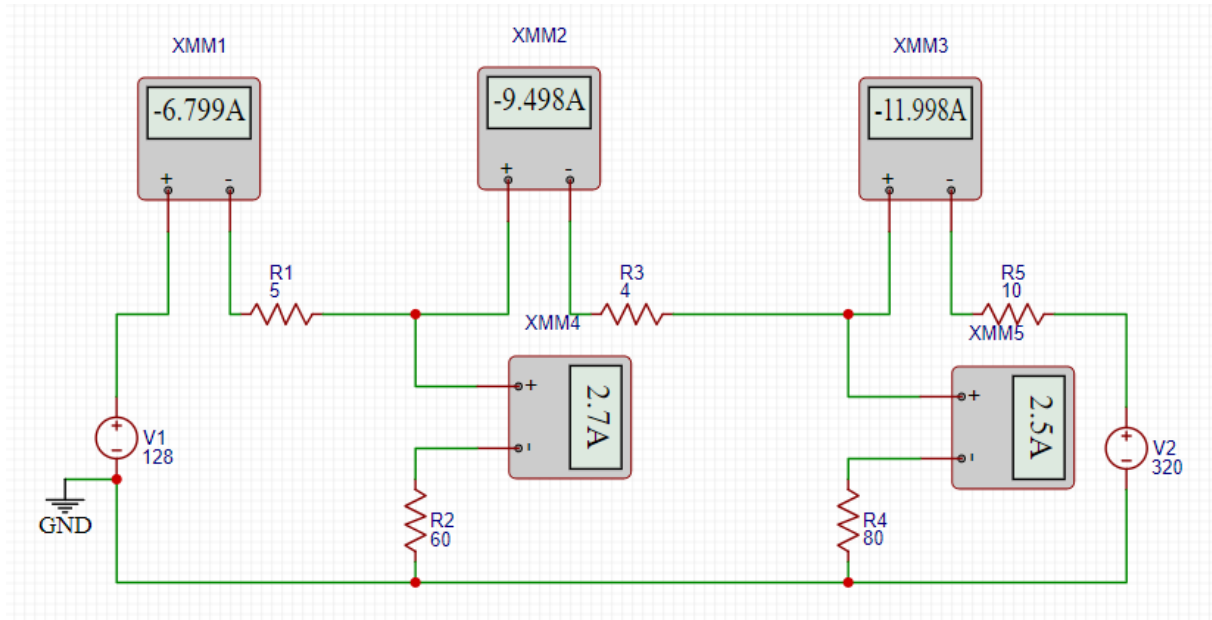


## 4.11.b

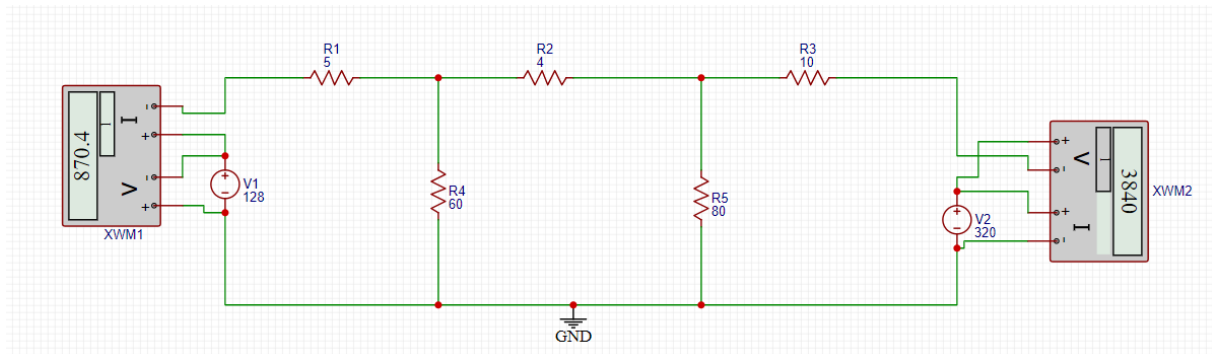


## 4.12

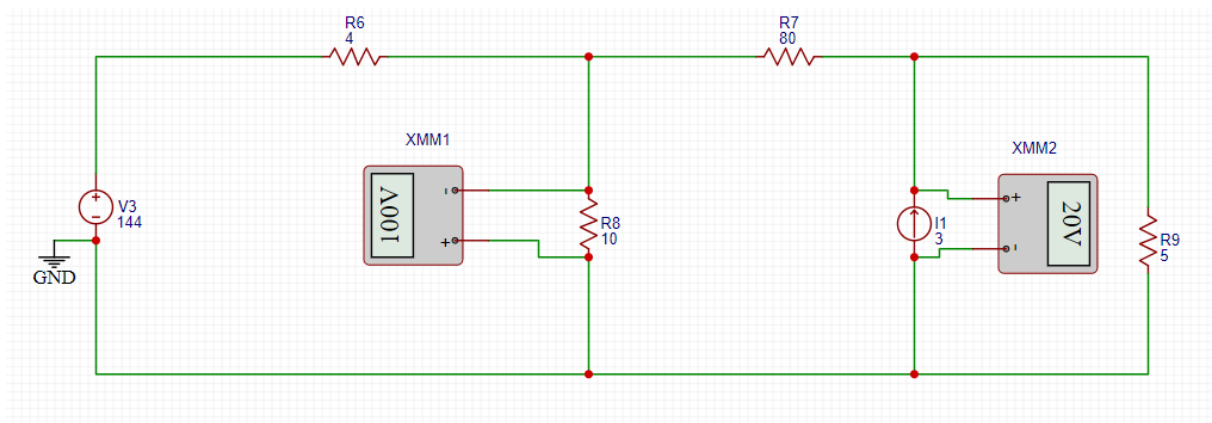

#### 4.15-a

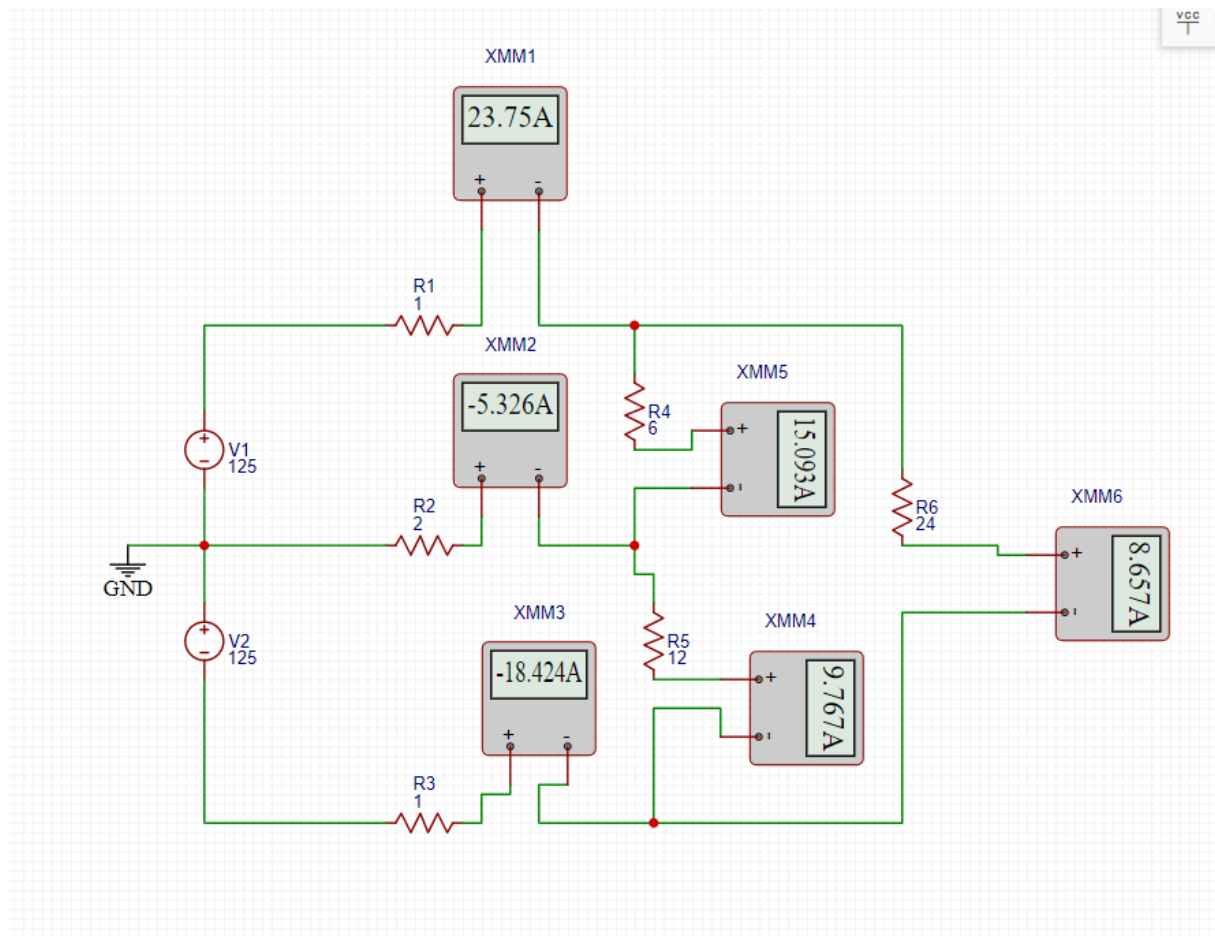


#### 4.15-b

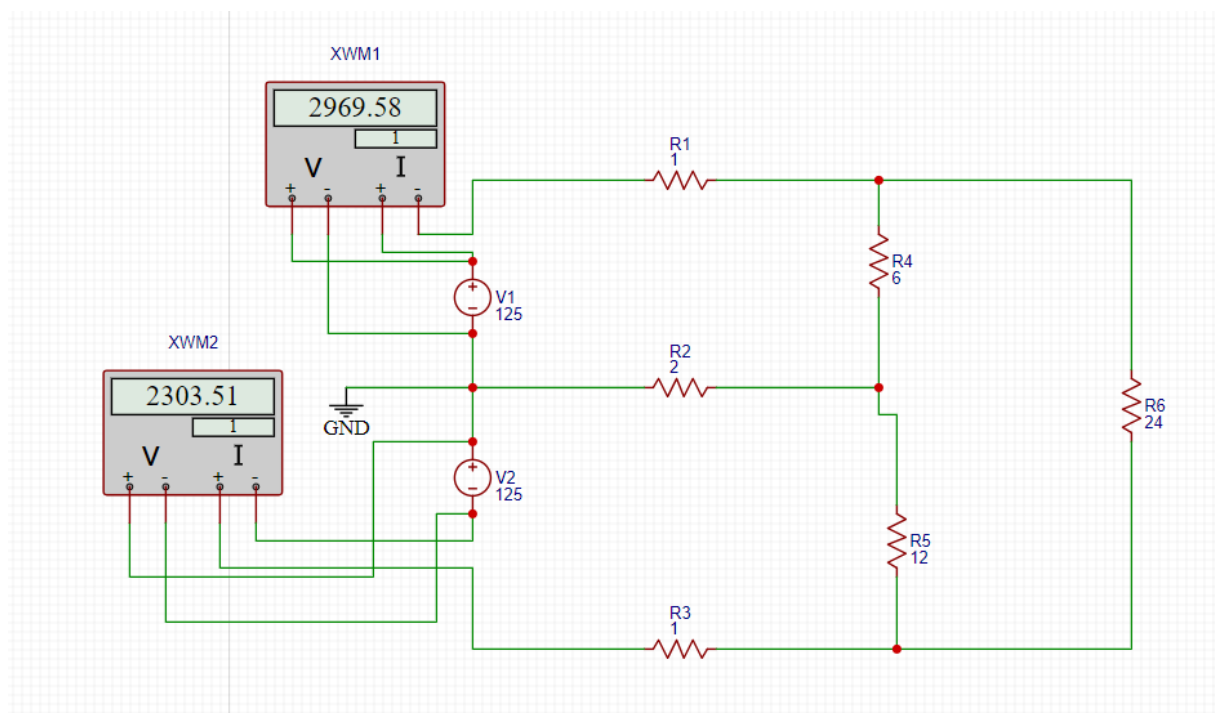





4.24

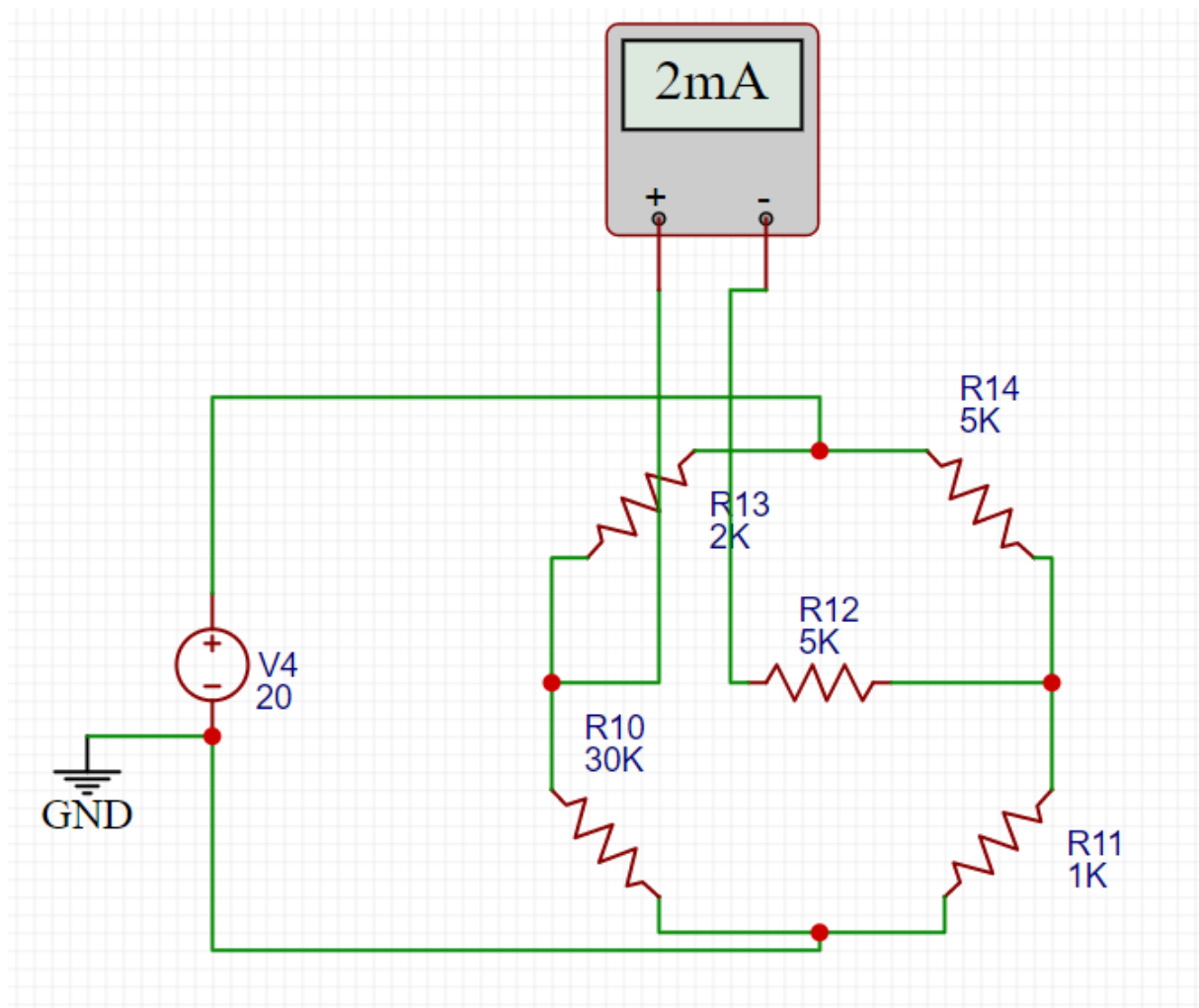


4.27

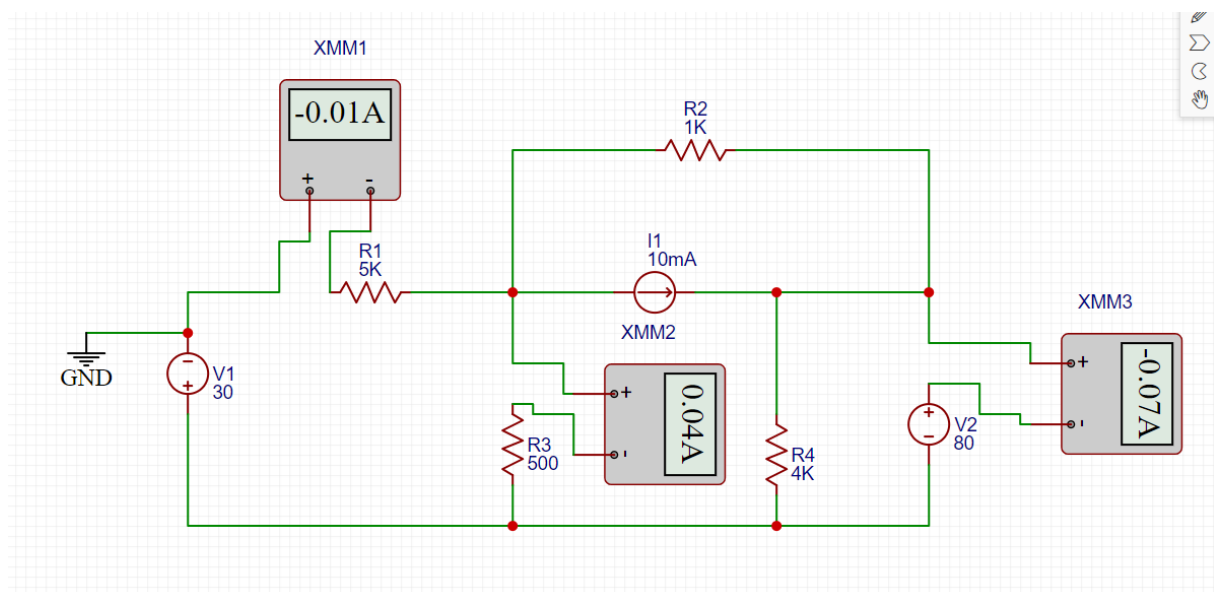

4.27.b

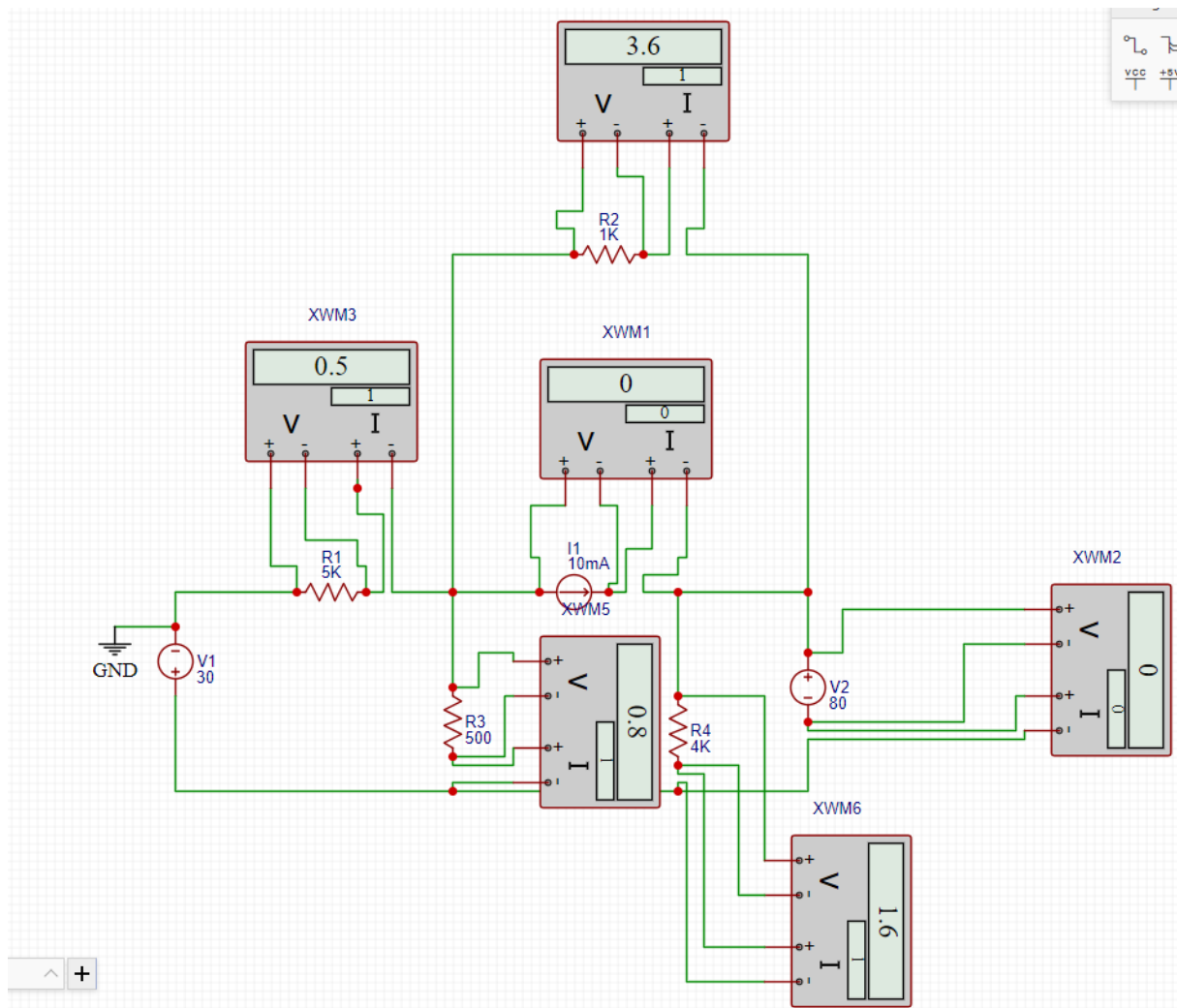


4.30

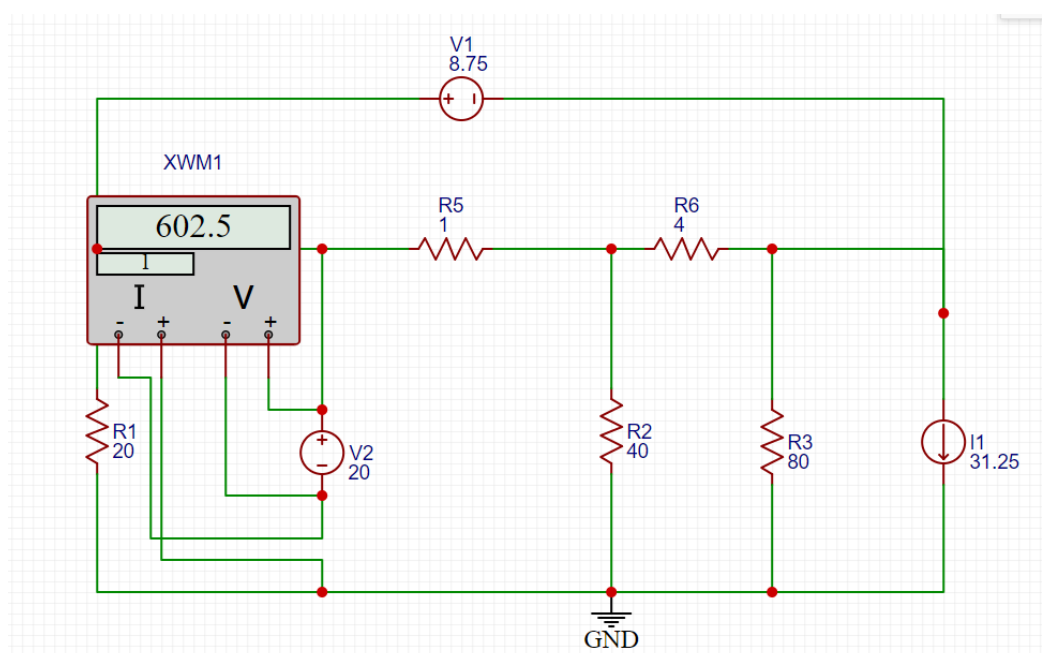





4.36

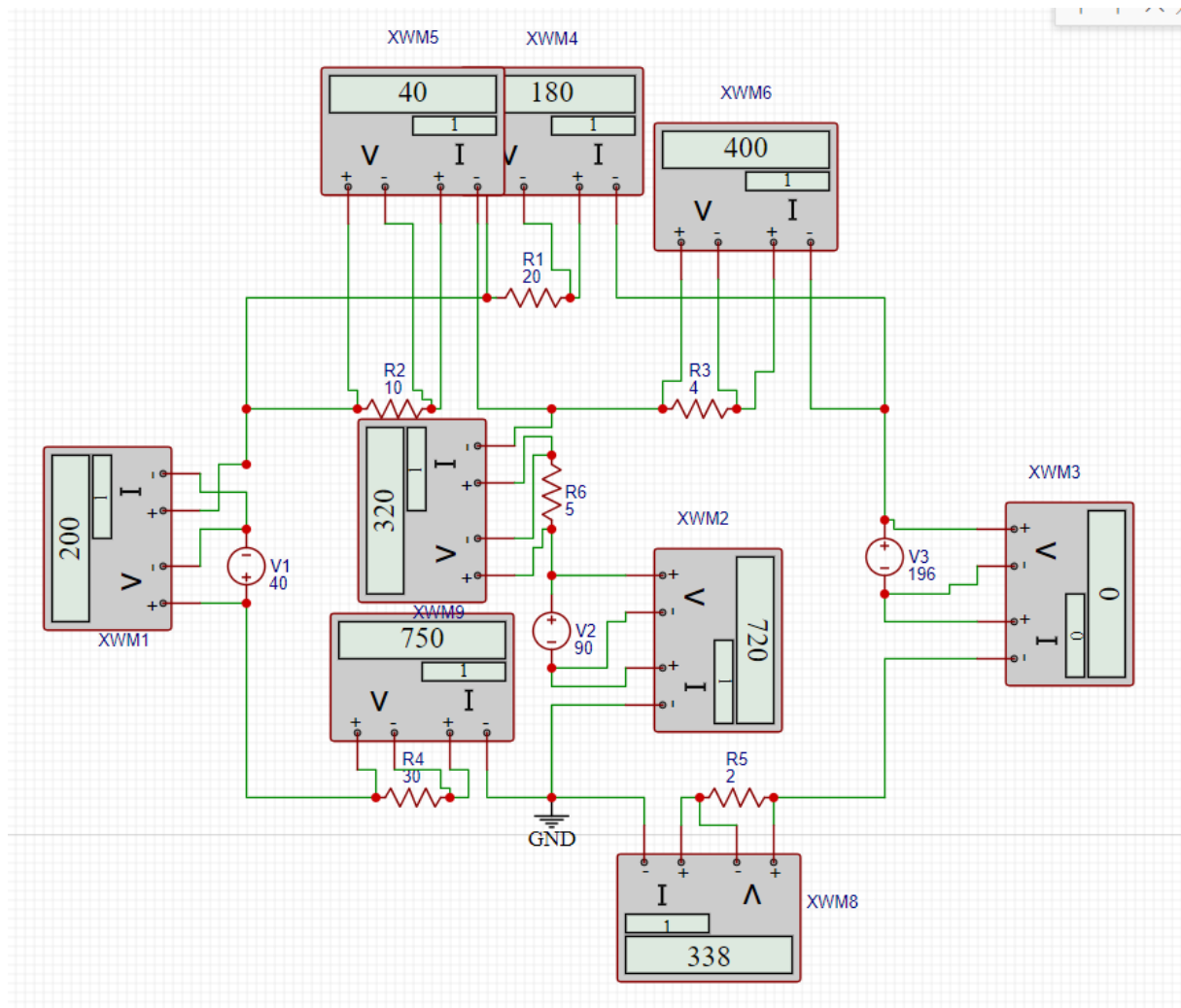


4.39

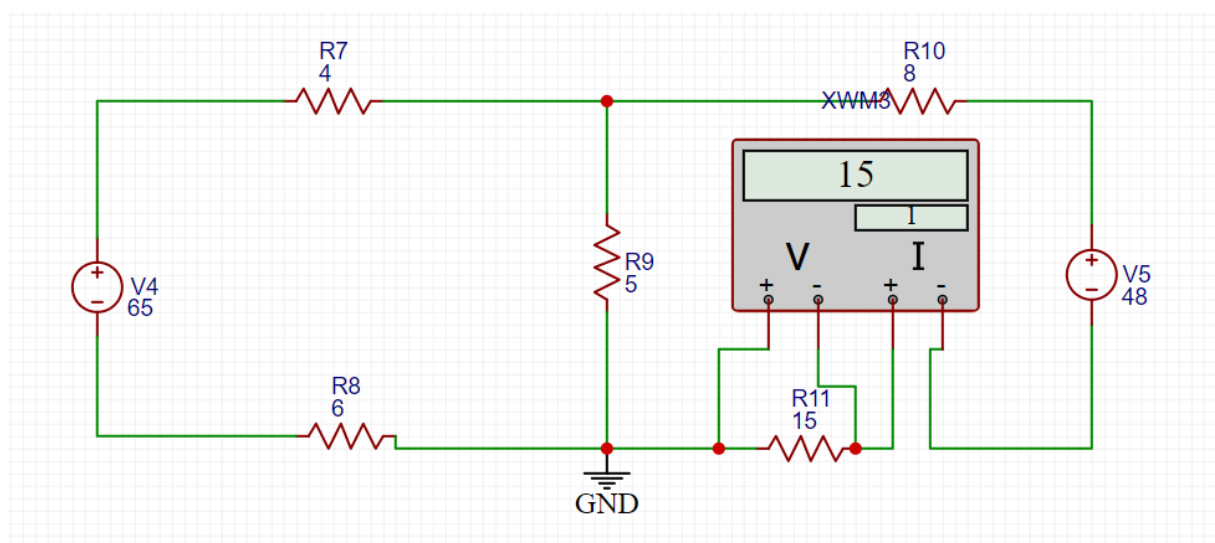

4.46

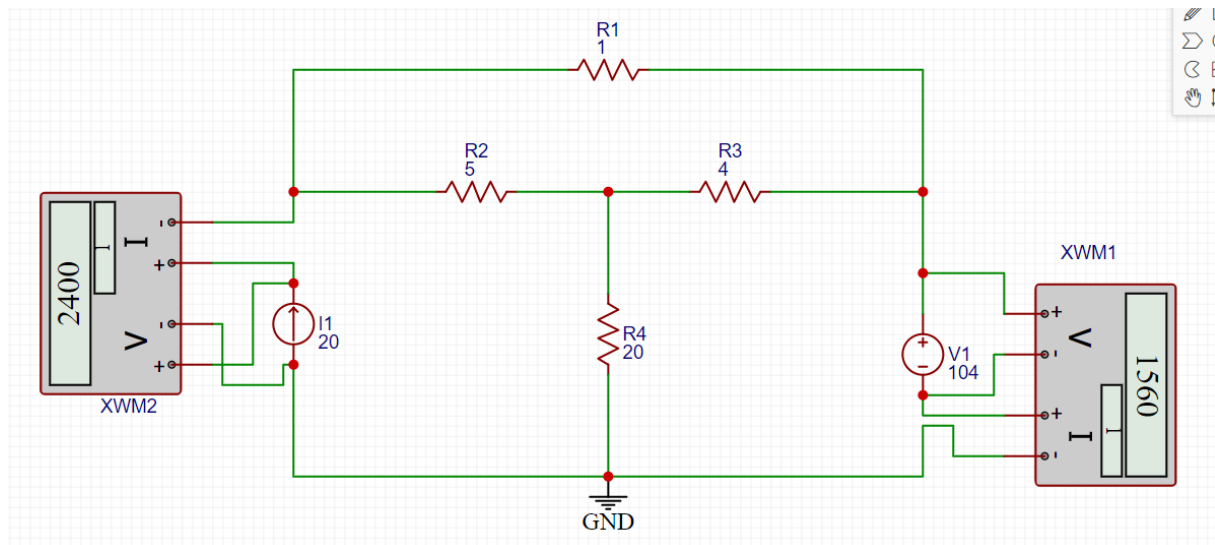


4.54

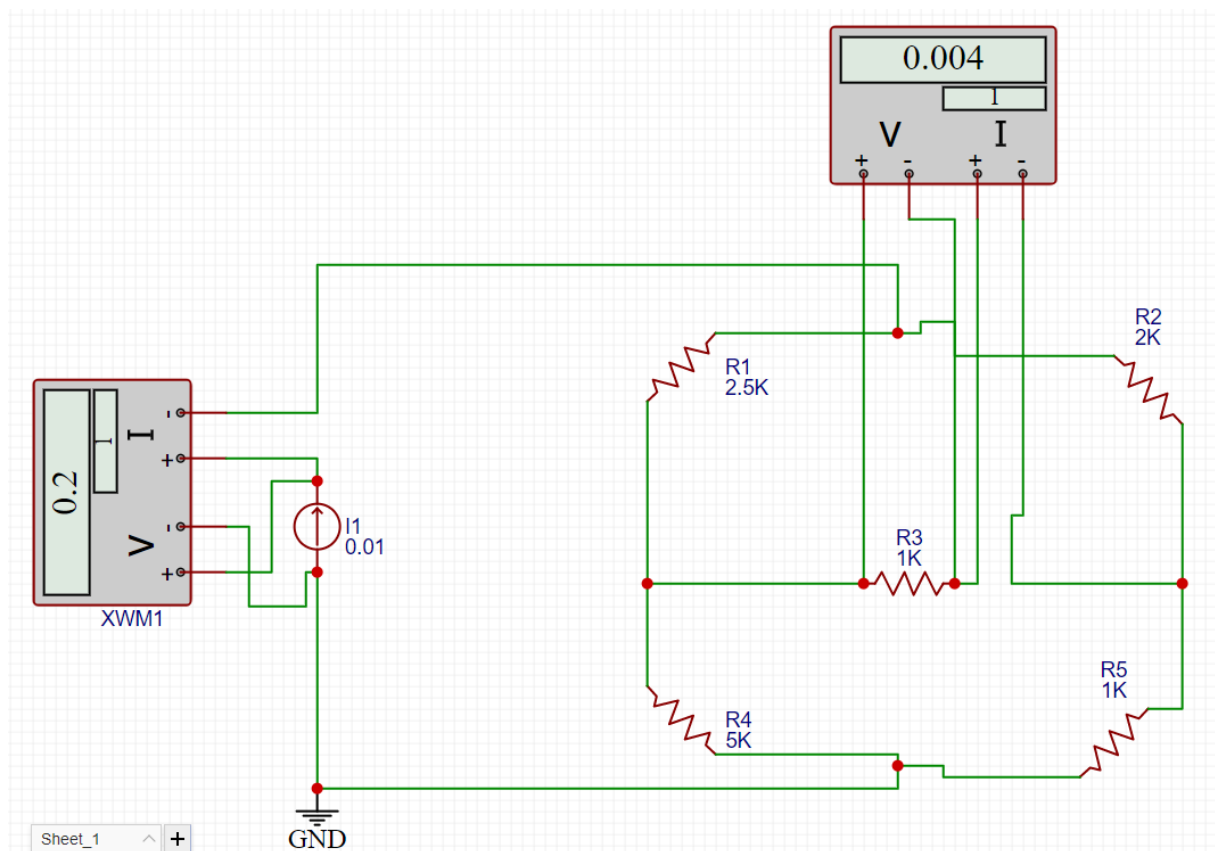




4.64

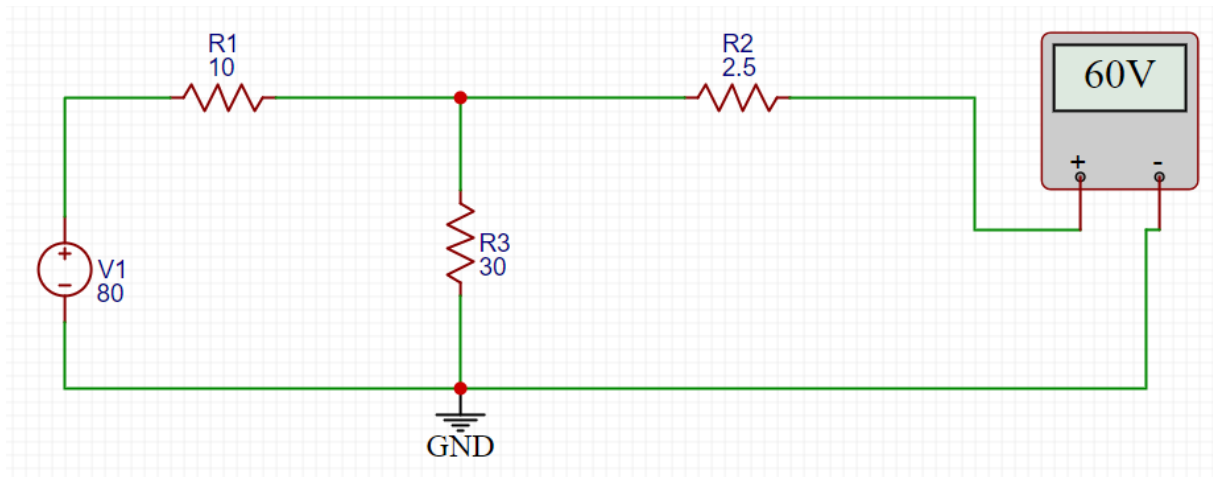

4.78

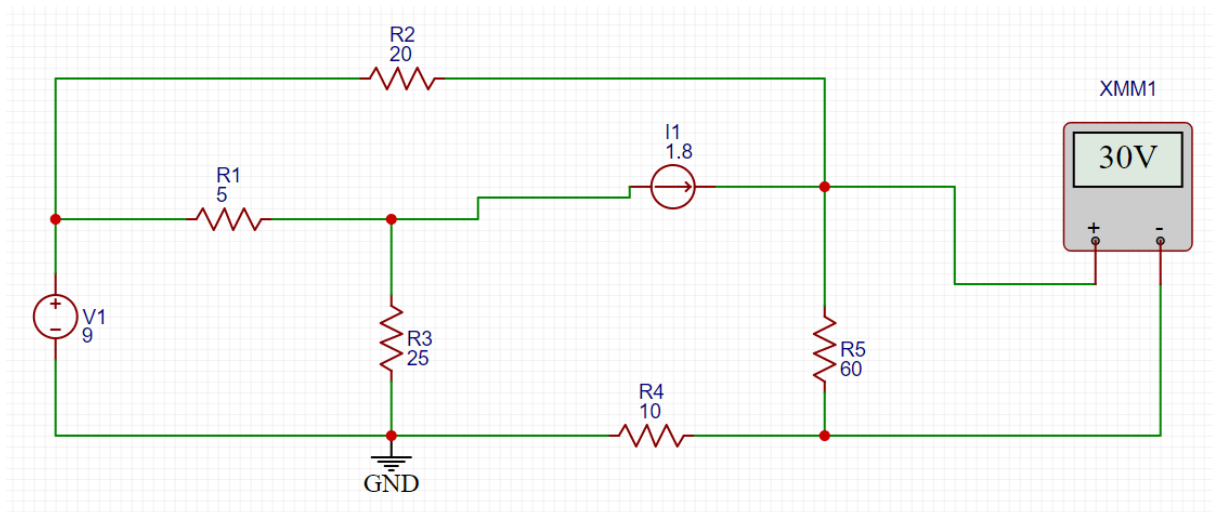

Barış Ayyıldız 1901042252