

CSE331 – Computer Organization

Lecture 5: Multiply, Shift and Divide


MULTIPLY (unsigned)

- ▶ Paper and pencil example (unsigned):

$$\begin{array}{rcl} \text{Multiplicand} & \longrightarrow & 1000 = 8 \\ \text{Multiplier} & \longrightarrow & \begin{array}{r} \times 1001 = 9 \\ \hline 1000 \\ 0000 \\ 0000 \\ 1000 \\ \hline 01001000 = 72 \end{array} \end{array}$$


- ▶ n bits \times n bits = $2n$ bit product
- ▶ Binary makes it easy:
 - 0 \Rightarrow place 0 (0 \times multiplicand)
 - 1 \Rightarrow place a copy (1 \times multiplicand)
- ▶ 4 versions of multiply hardware & algorithm:
 - **successive refinement**

Conventional Array Multiplier

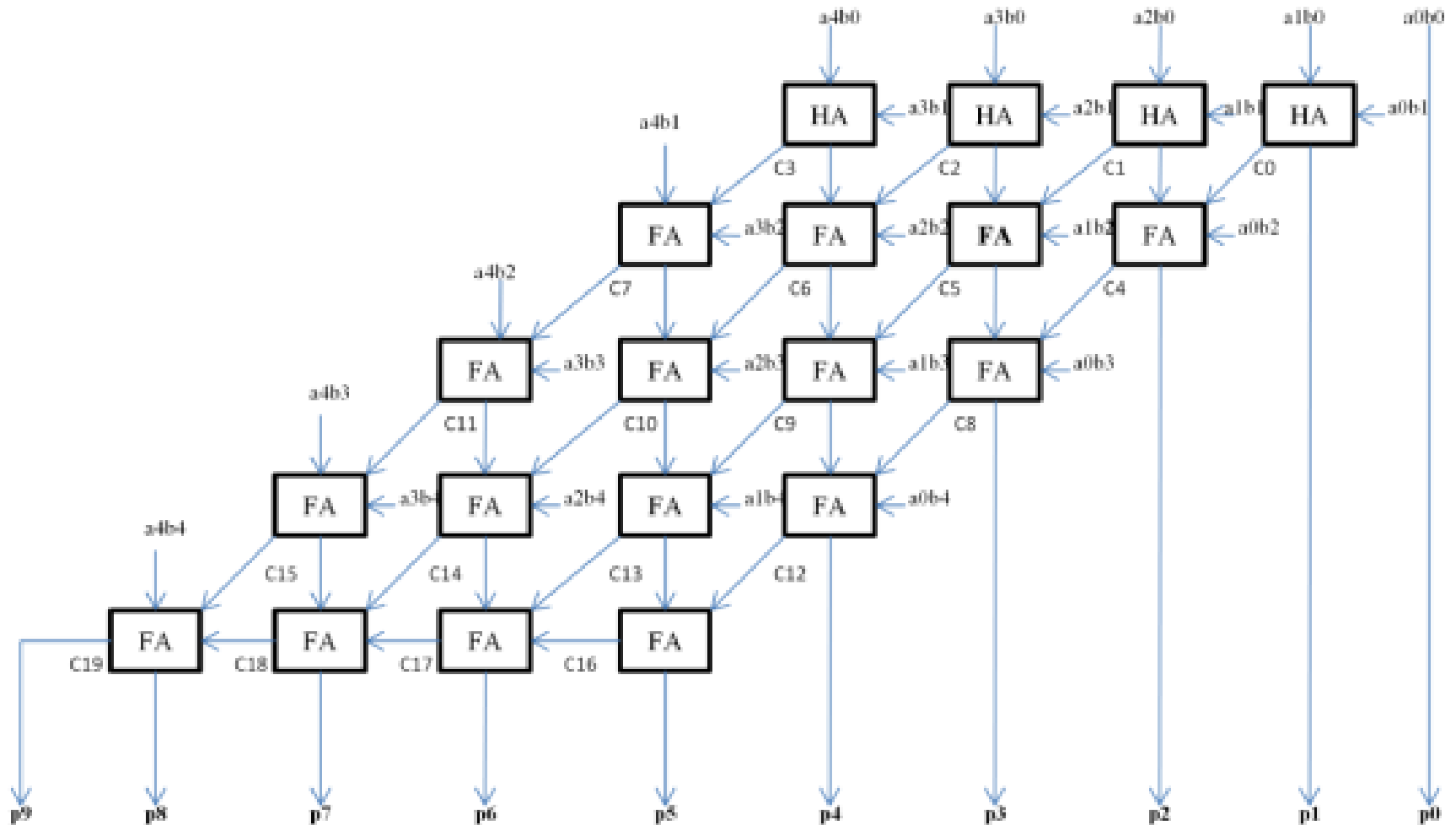


Unsigned shift-add multiplier (version 1)

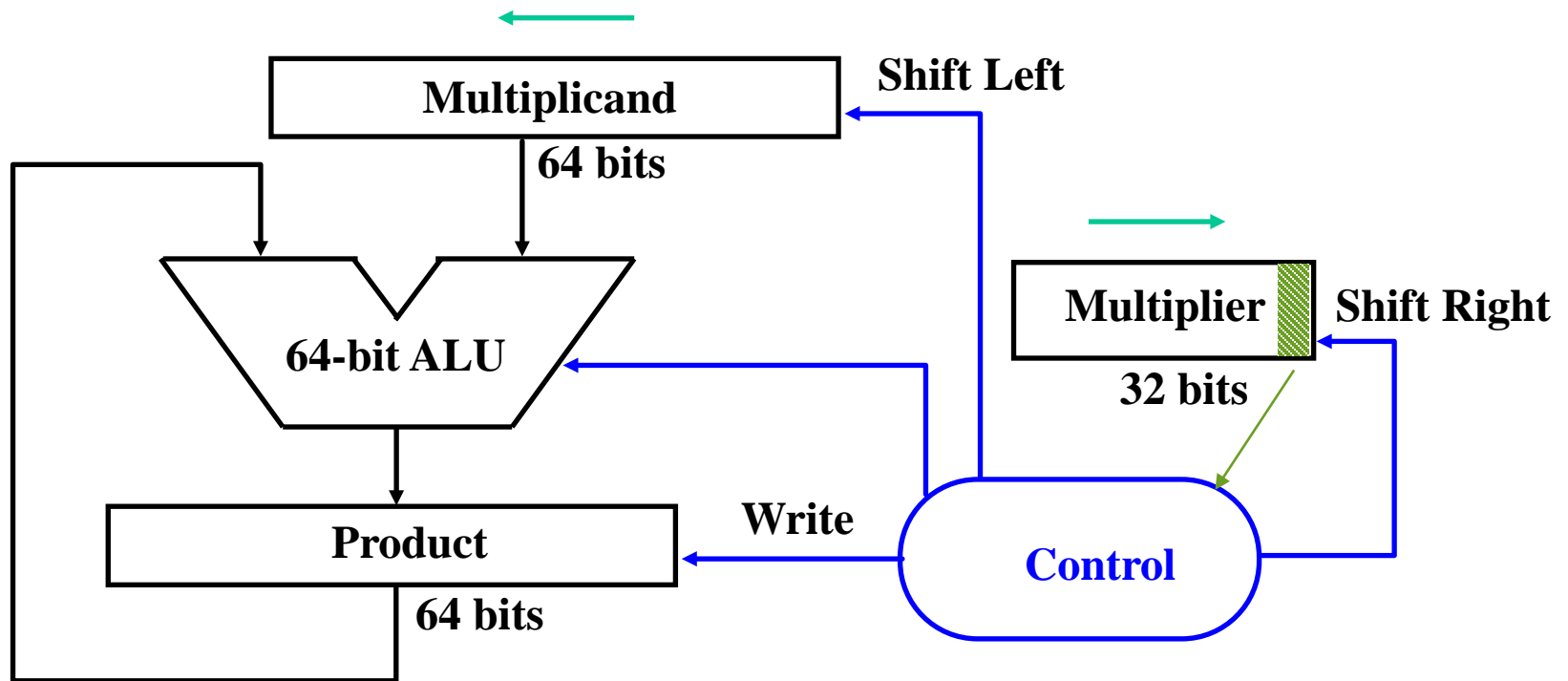- ▶ 64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit multiplier reg



Multiplier = datapath + control

Multiply Algorithm Version 1

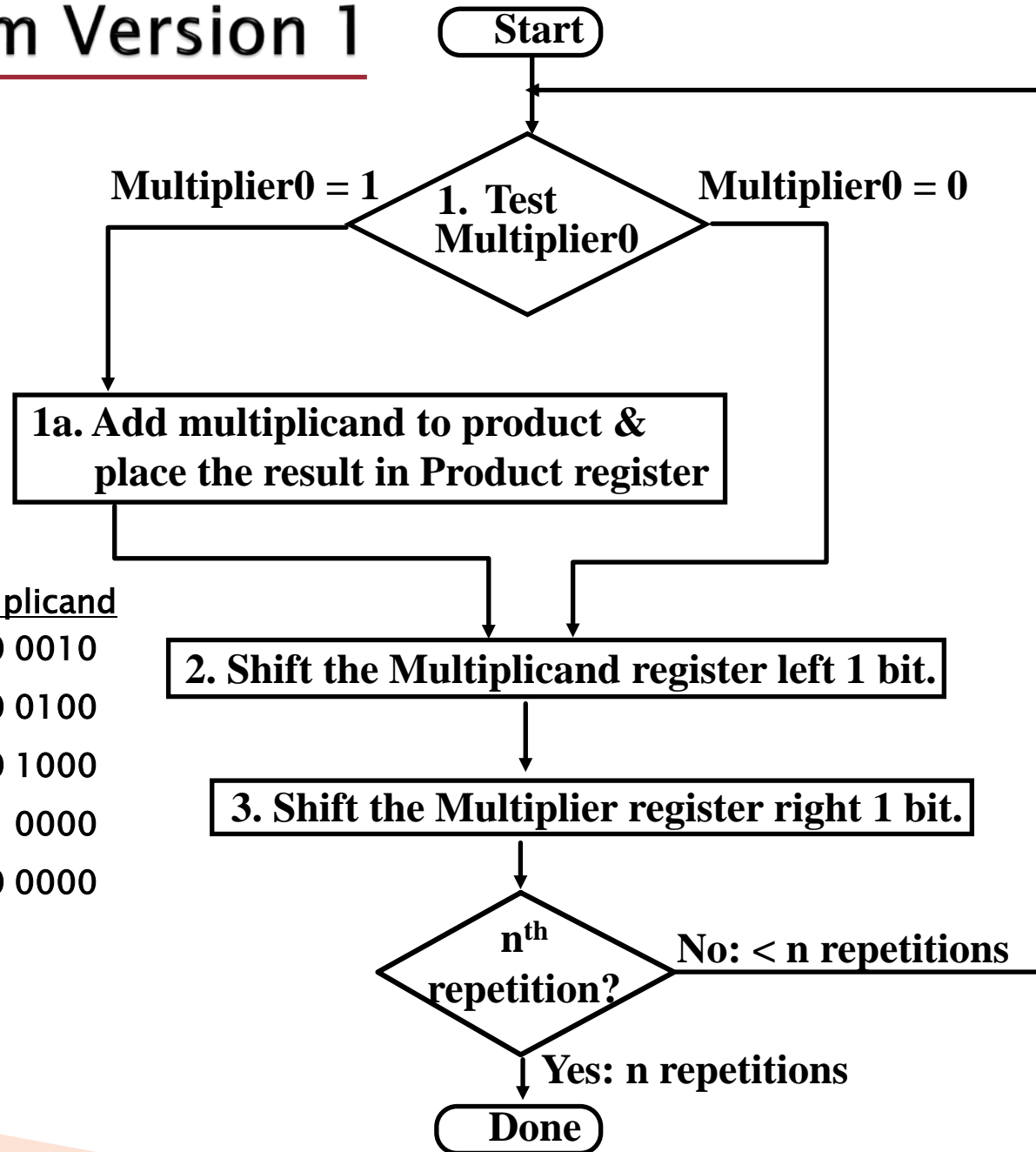


<u>Product</u>	<u>Multiplier</u>	<u>Multiplicand</u>
0000 0000	0011	0000 0010
0000 0010	0001	0000 0100
0000 0110	0000	0000 1000
0000 0110	0000	0001 0000
0000 0110	0000	0010 0000
0000 0110		

Observations on Multiply Version 1


- ▶ 1 / 2 bits in multiplicand always 0
=> 64-bit adder is wasted
- ▶ 0's inserted into the least significant bit of multiplicand as shifted => least significant bits of product never changed once formed
- ▶ Instead of shifting multiplicand to left, shift product to right.

MULTIPLY HARDWARE Version 2

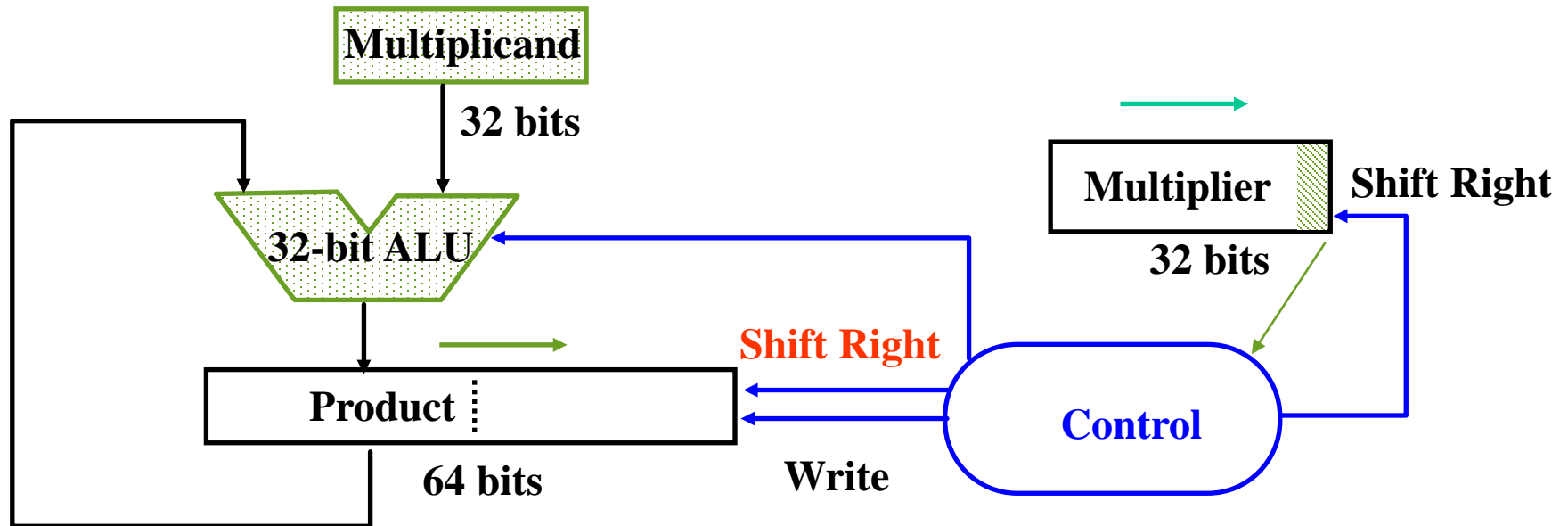
- ▶ 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, 32-bit Multiplier reg




Multiply Algorithm Version 2

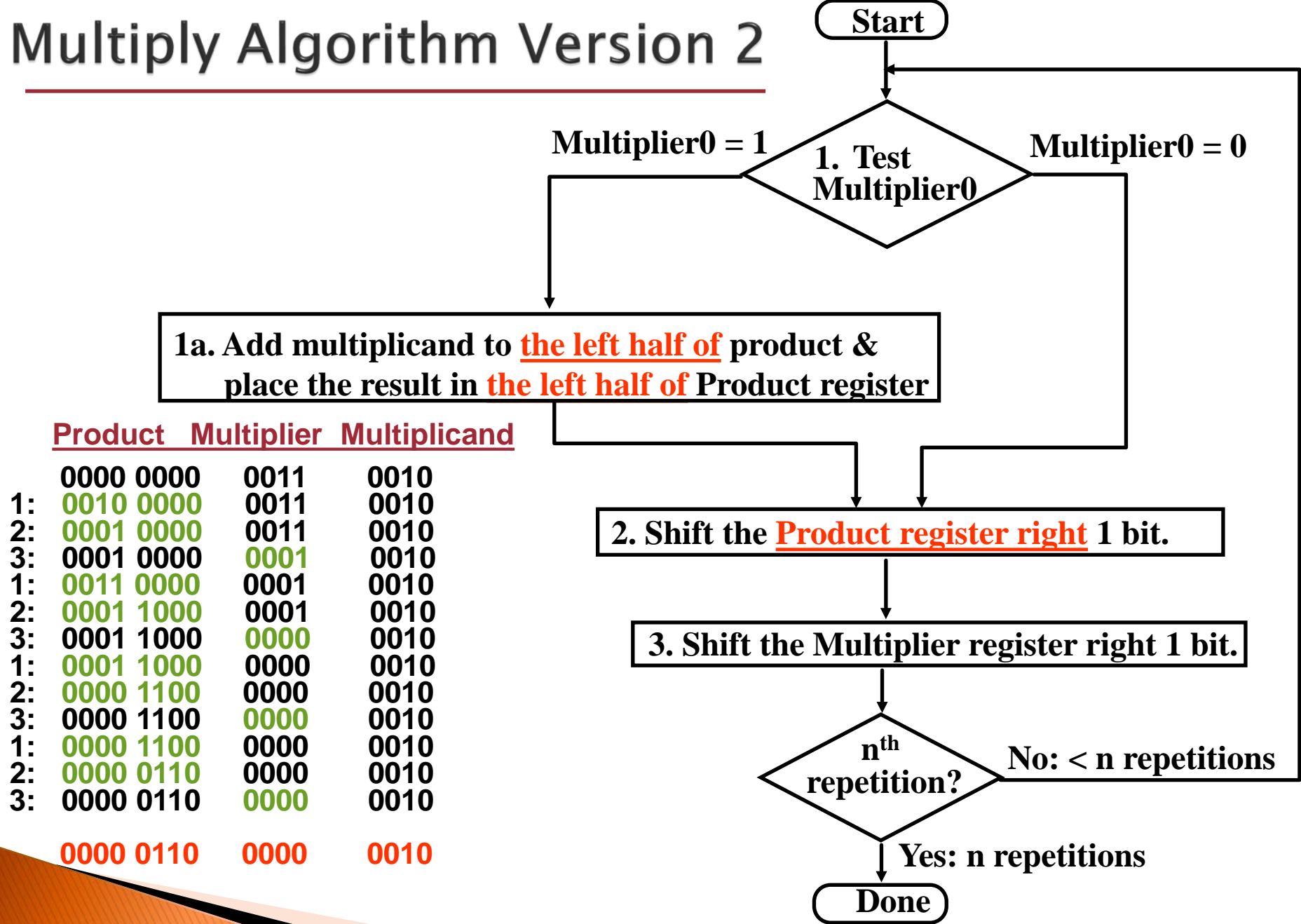

Still more wasted space!

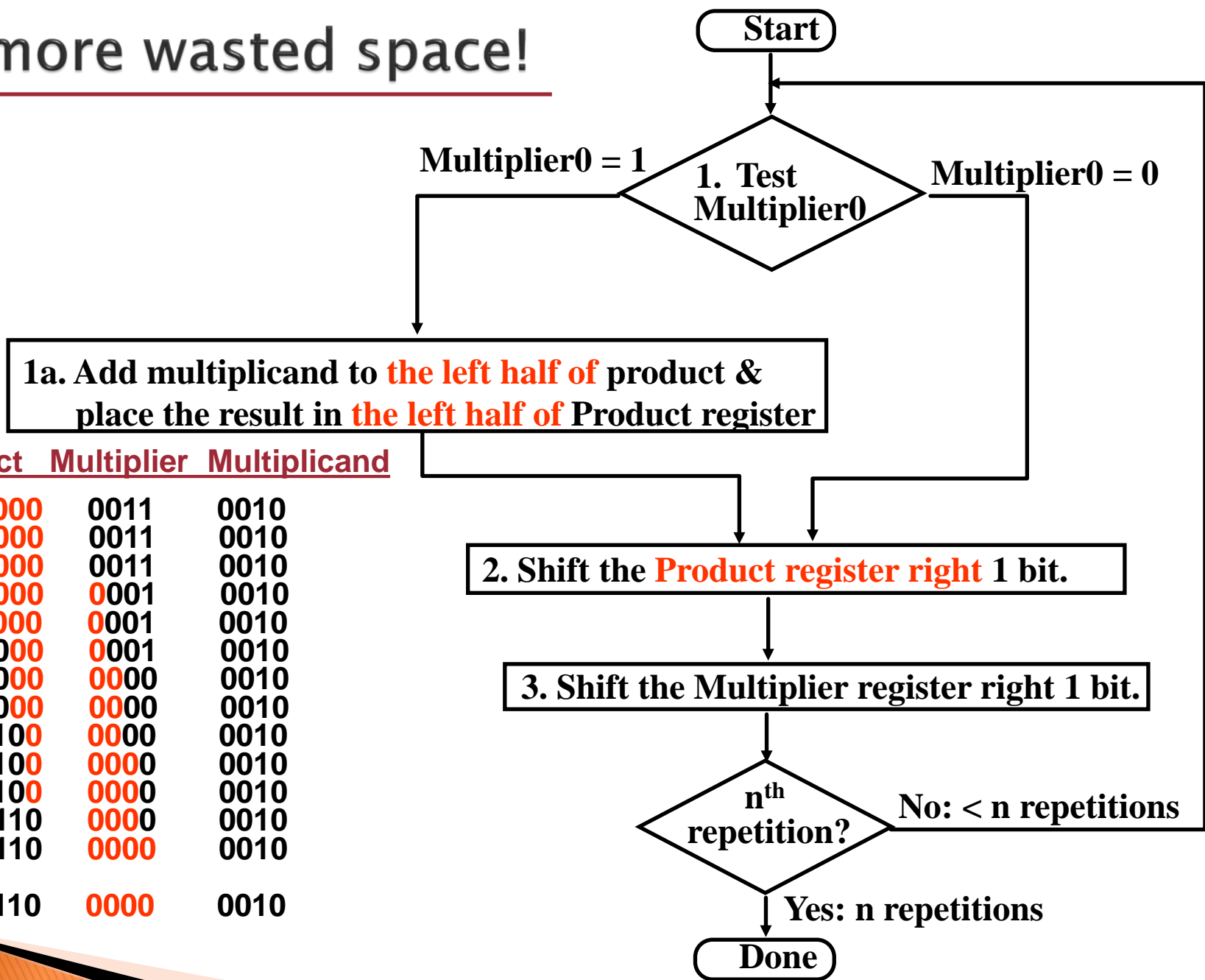


Observations on Multiply Version 2

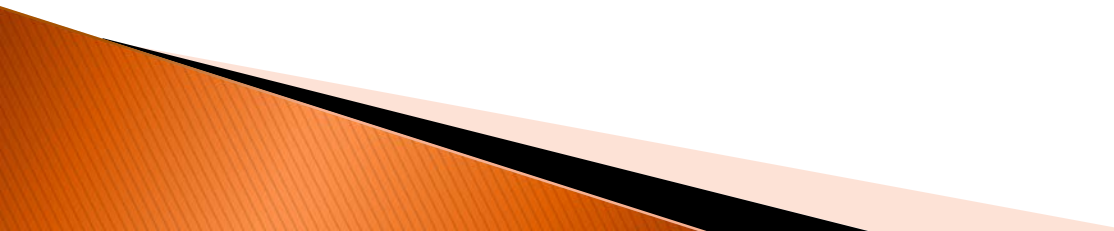- ▶ Product register wastes space that exactly matches size of multiplier
 - ▶ Both Multiplier register and Product register require right shift
 - ▶ Combine Multiplier register and Product register
- 

MULTIPLY HARDWARE Version 3

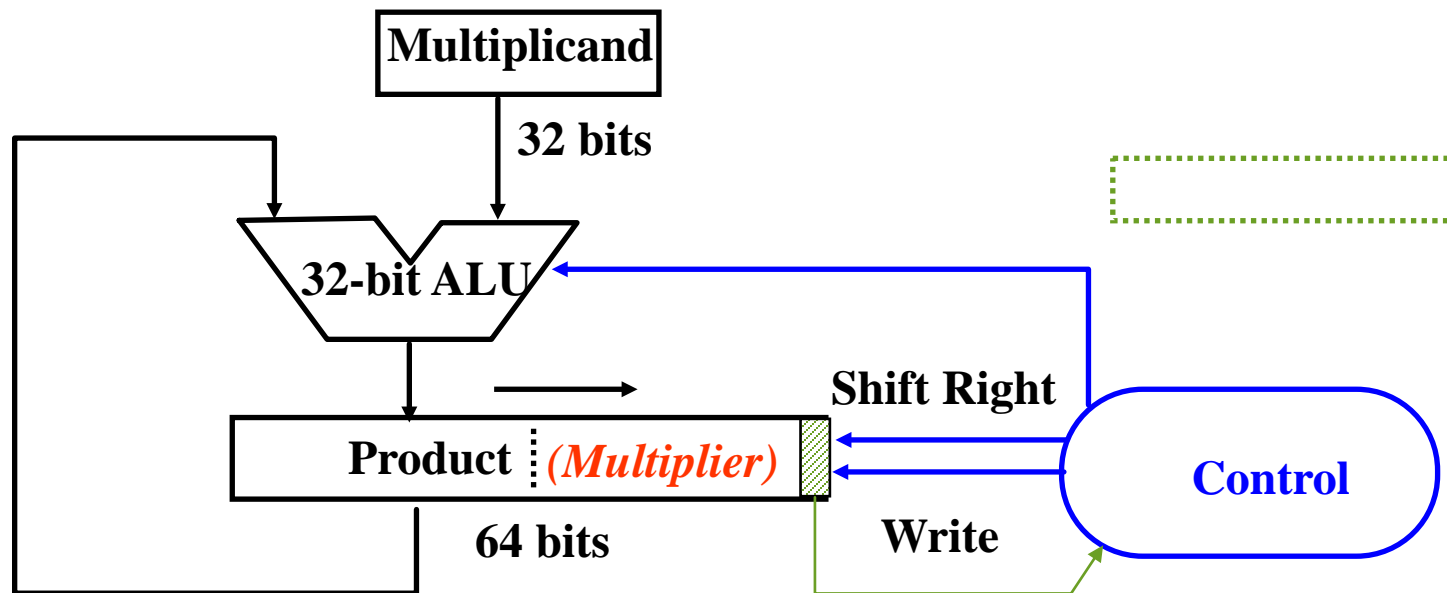- ▶ 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, (0-bit Multiplier reg)



Multiply Algorithm Version 3

MultiplicandMultiplier

0010

0011

1a. Add multiplicand to the left half of product & place the result in the left half of Product register

	<u>Product</u>	<u>Multiplicand</u>
	0000 0011	0010
1:	0010 0011	0010
2:	0001 0001	0010
1:	0011 0001	0010
2:	0001 1000	0010
1:	0001 1000	0010
2:	0000 1100	0010
1:	0000 1100	0010
2:	0000 0110	0010
	0000 0110	0010

Product0 = 1

1. Test
Product0

Product0 = 0

2. Shift the Product register right 1 bit.

32nd
repetition?

No: < 32 repetitions

Yes: 32 repetitions

Done

Observations on Multiply Version 3

- ▶ 2 steps per bit because Multiplier & Product combined
- ▶ MIPS registers Hi and Lo are left and right half of Product
- ▶ Gives us MIPS instruction Multu
- ▶ What about signed multiplication?
 - easiest solution is to make both positive & remember whether to complement product when done (leave out the sign bit, run for 31 steps)
 - Booth's Algorithm is elegant way to multiply signed numbers using same hardware as before and save cycles
 - can be modified to handle multiple bits at a time

Motivation for Booth's Algorithm

- ▶ Example $2 \times 6 = 0010 \times 0110$:

	0010	
x	0110	
+	0000	shift (0 in multiplier)
+	0010	add (1 in multiplier)
+	0010	add (1 in multiplier)
+	0000	shift (0 in multiplier)
	<u>00001100</u>	


- ▶ ALU with add or subtract gets same result in more than one way:

$$\begin{aligned}
 12 &= -4 + 16 \\
 01100 &= -00100 + 10000
 \end{aligned}$$

- ▶ For example

	0010	
x	0110	
	<u>0000</u>	shift (0 in multiplier)
	-0010	sub (start string of 1's)
	0000	shift (mid string of 1's)
	+ 0010	add (end string of 1's)
	<u>00001100</u>	

Booth's Algorithm

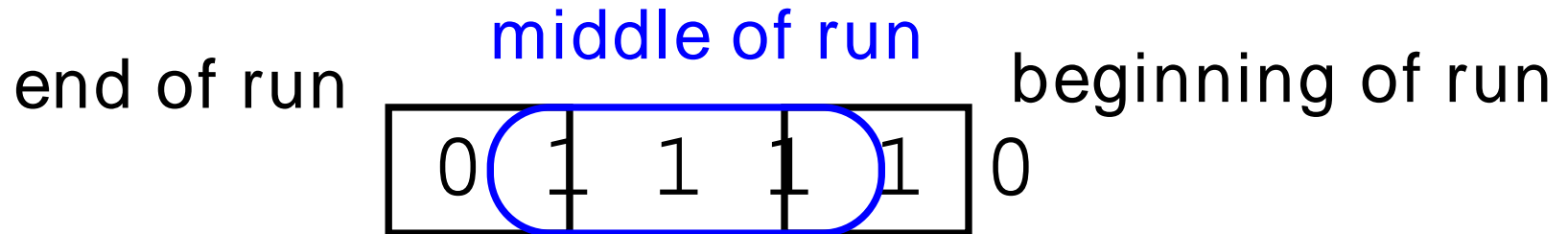

<u>Current Bit</u>	<u>Bit to the Right</u>	<u>Explanation</u>	<u>Example</u>	<u>Op</u>
1	0	Begins run of 1s	000111 <u>1</u> 000	sub
1	1	Middle of run of 1s	00011 <u>11</u> 000	none
0	1	End of run of 1s	00 <u>01</u> 111000	add
0	0	Middle of run of 0s	0 <u>00</u> 1111000	none

Originally for Speed (when shift was faster than add)

- Replace a string of 1s in multiplier with an initial subtract when we first see a one and then later add for the bit after the last one

Booths Example (2 x 7)

<u>Operation</u>	<u>Multiplicand</u>	<u>Product</u>	<u>next?</u>
0. initial value	0010	0000 0111 0	10 -> sub
1a. $P = P - m$	1110	+ 1110 1110 0111 0	shift P (sign ext)
1b.	0010	1111 0011 1	11 -> nop, shift
2.	0010	1111 1001 1	11 -> nop, shift
3.	0010	1111 1100 1	01 -> add
4a.	0010	+ 0010 0001 1100 1	shift
4b.	0010	0000 1110 0	done

Booths Example (2 x -3)

<u>Operation</u>	<u>Multiplicand</u>	<u>Product</u>	<u>next?</u>
0. initial value	0010	0000 1101 0	10 -> sub
1a. $P = P - m$	1110	+ 1110 1110 1101 0	shift P (sign ext)
1b.	0010	1111 0110 1 + 0010	01 -> add
2a.		0001 0110 1	shift P
2b.	0010	0000 1011 0 + 1110	10 -> sub
3a.	0010	1110 1011 0	shift
3b.	0010	1111 0101 1	11 -> nop
4a		1111 0101 1	shift
4b.	0010	1111 1010 1	done


Shifters

Two kinds:

logical-- value shifted in is always "0"



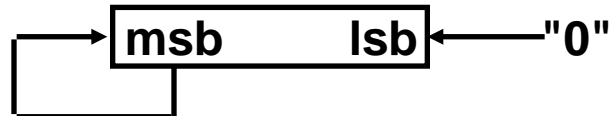
arithmetic-- on right shifts, sign extend




Note: these are single bit shifts. A given instruction might request 0 to 32 bits to be shifted!

Combinational Shifter from MUXes

Basic Building Block

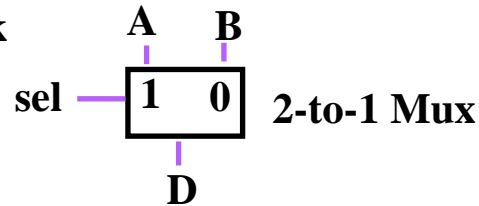

8-bit right shifter

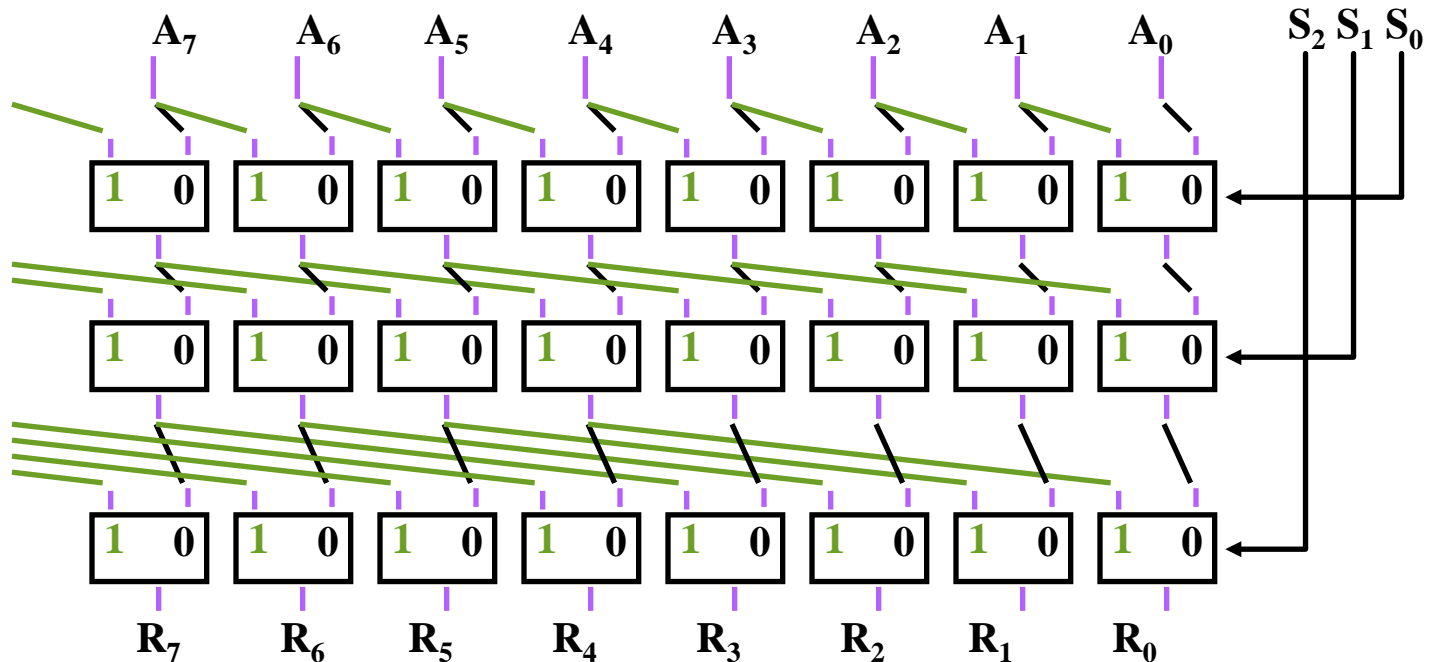

- ▶ What comes in the MSBs?
- ▶ How many levels for 32-bit shifter?